



ANALOG SIGNAL PROCESSING



ECE 210 & 211

Exercise 1

7st March, 2023

Prof. Yang Xu (徐杨)

yangxu-isee@zju.edu.cn

Yue Dai, yuedai@zju.edu.cn
 Jinfeng Huang, huangjinfeng@zju.edu.cn
 Yance Chen, 12031045@zju.edu.cn
 Yuan Ma, 22241064@zju.edu.cn
 Youshui He, 22241003@zju.edu.cn

Zongwen Li, zongwen_li@zju.edu.cn
 Muhammad Malik, mmalik@zju.edu.cn
 Munir Ali, Munir_li@zju.edu.cn
 Muhammad Abid, abid_anwar@zju.edu.cn

$\rightarrow =$
 $\begin{matrix} + & + & - \\ - & & - \end{matrix}$
 $|kI_x$




ZJU-UIUC Institute

Zhejiang University / University of Illinois at Urbana-Champaign Institute



Question 1 a: Find I_o in the network in network given below? $I_o = -48 \text{ mA}$

I_o

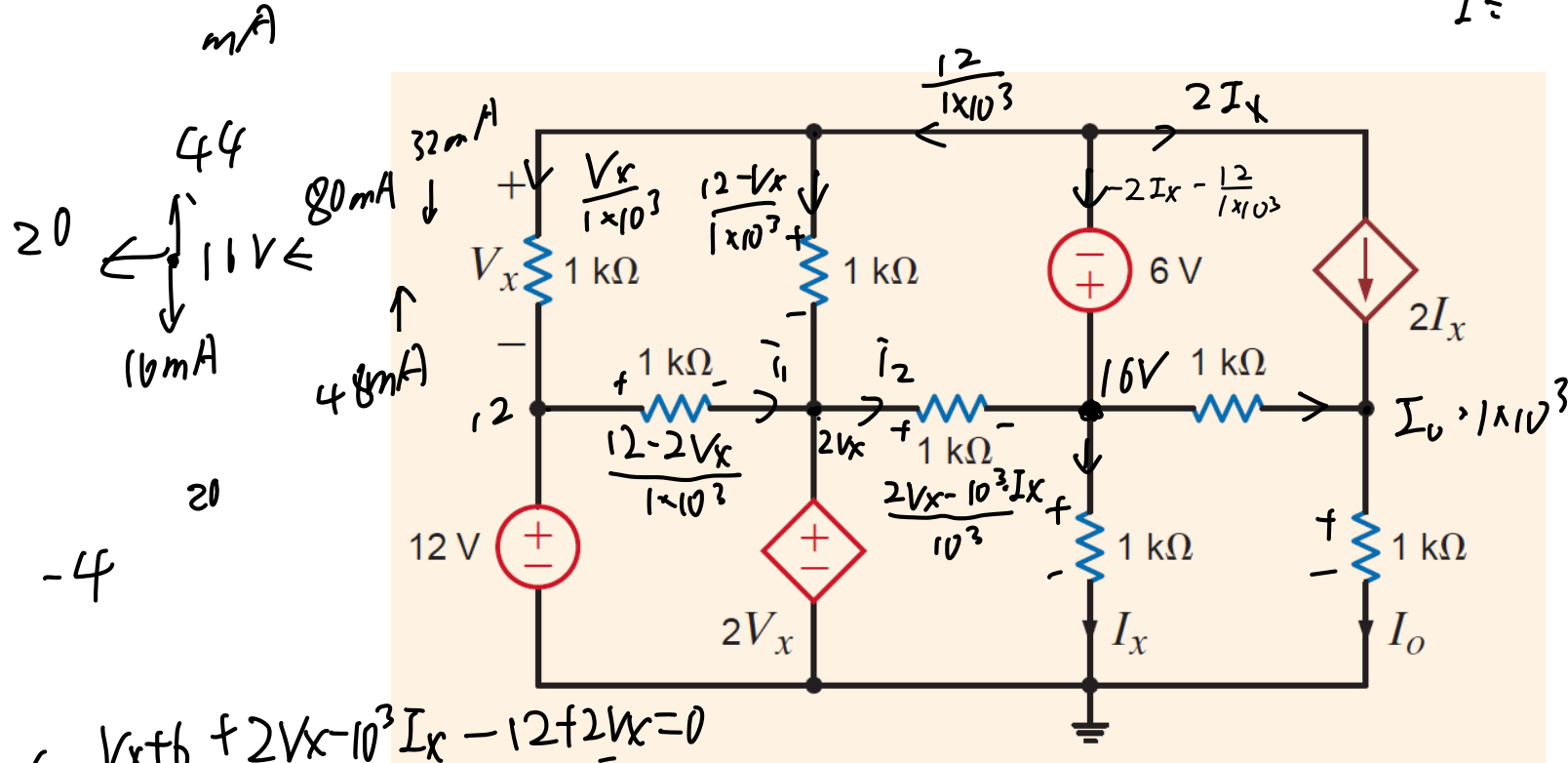

$$I_x = \frac{16}{10^3} A$$

$$-2 \cdot \frac{16}{10^3} - \frac{12}{1 \times 10^3}$$

$$= \frac{-44}{10^3}$$

$$= -32 \cdot 12$$

$$2V_x - 18 - V_x$$

$$18 + V_x$$

$$V_x + 6 + 2V_x - 10^3 I_x - 12 + 2V_x = 0$$

$$18 + V_x + 10^3 I_x = 0$$

$$\frac{12 + V_x + 6}{1 \times 10^3} + \frac{18 + V_x - 10^3 I_o}{10^3} = \frac{V_x - 18}{10^3} - 2I_x - \frac{12}{10^3}$$

$$10^3 I_x = -V_x - 12$$

$$5V_x - 6 + V_x + 12 = 0$$

$$6V_x = -12$$

$$V_x = -2V$$

$$I_a = \frac{V_x}{2} \text{ mA}$$

$$I_b = 4 - \frac{V_x}{2} \text{ mA}$$

$$12 + 10^3 I_x \text{ mA}$$

$$10^3 I_x - V_x - 10^3 I_x - 12 = 0$$

$$V_x = -12V$$


$$I_a = 6 \text{ mA}$$

$$I_1 = 4 \text{ mA}$$

$$I_2 = -6 \text{ mA}$$

$$I_3 = -2 \text{ mA}$$

$$I_4 = -10 \text{ mA}$$

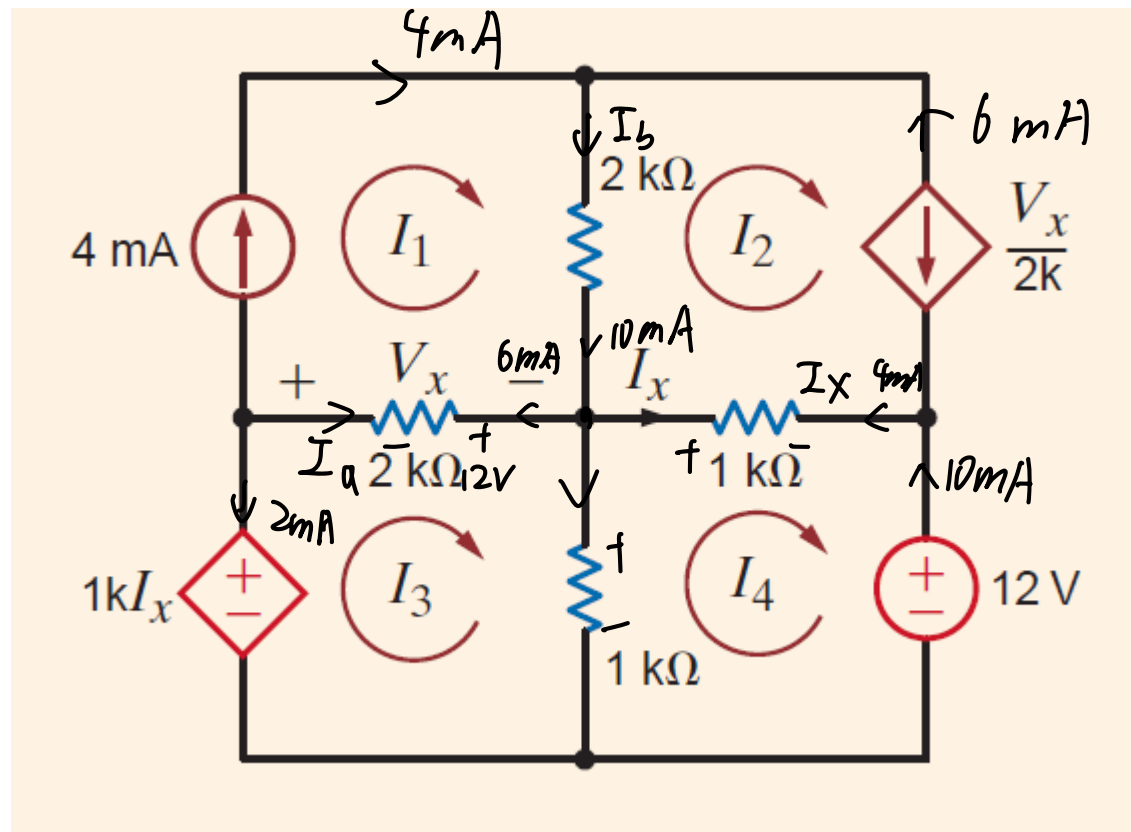

$$12V + 10^3 I_x = \left(\frac{4}{10^3} - I_x \right) 10^3$$

Question 2 : Determine V_o in the circuit using Thevenin theorem?

$$V_o = \frac{33}{4} \text{ V}$$

$$= 4 - 10^3 I_x$$

$$2 \cdot 10^3 I_x = -8 - 4$$

$$I_x = -4 \text{ mA}$$

Assume $V_1 = 0 \text{ V}$

KCL for node 3

$$\frac{V_x}{2} = 2 + \frac{V_x}{4}$$


$$\Rightarrow V_x = 8 \text{ V}$$

$$I_1 = 4 \text{ mA}$$

KCL for node 0

$$4 = \frac{V_o - 3}{2} + \frac{V_o - 0}{6}$$

$$\Rightarrow V_o = \frac{33}{4} \text{ V}$$

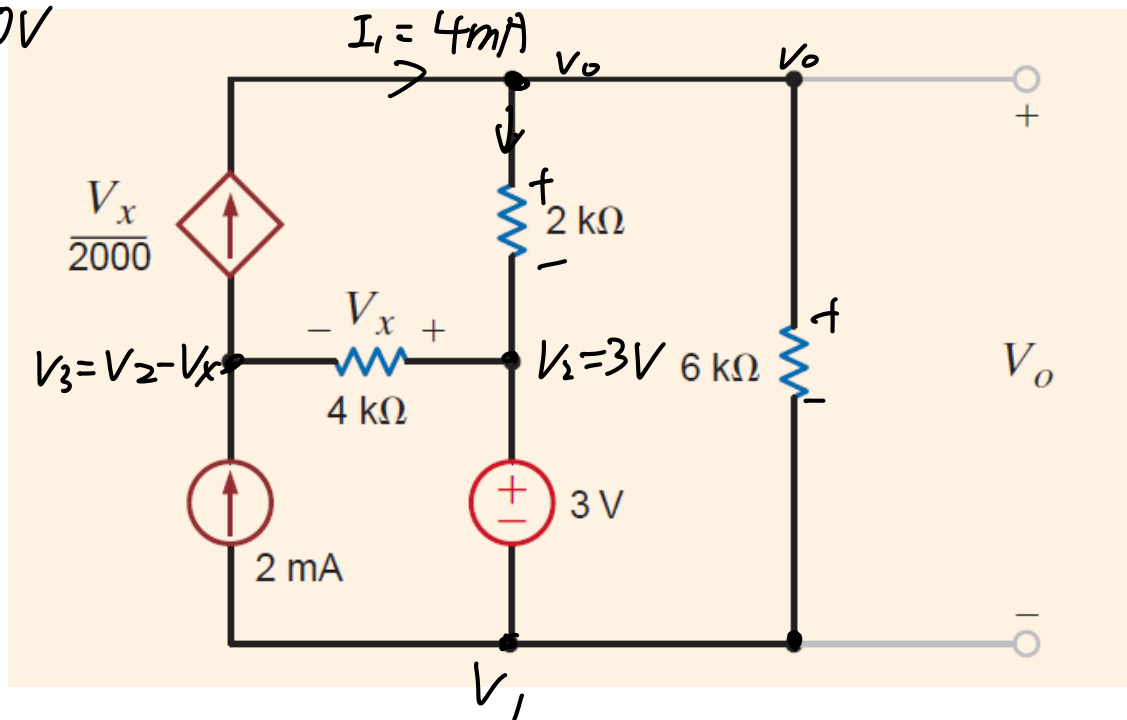

Question 3 :


The two op-amp circuits shown produce an output given by the equation

$$V_o = 8V_1 - 4V_2$$

where

$$1\text{ V} \leq V_1 \leq 2\text{ V} \quad \text{and} \quad 2\text{ V} \leq V_2 \leq 3\text{ V}$$

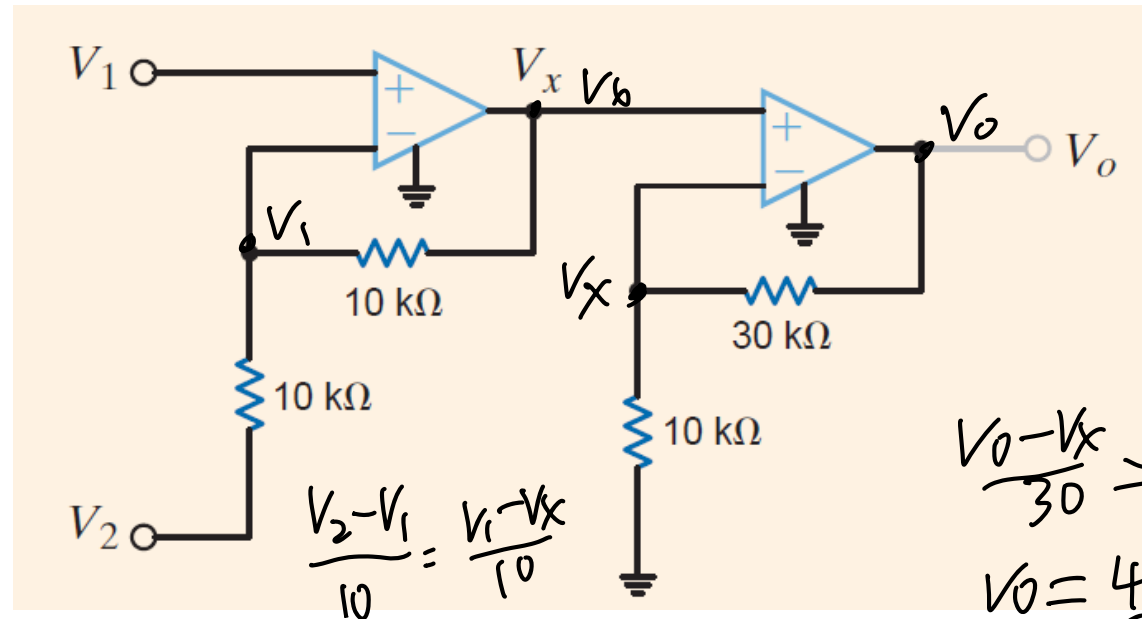We wish to determine (a) the range of V_o and (b) if both of the circuits will produce the full range of V_o given that the dc supplies are $\pm 10\text{ V}$.



$$V_o \in [-4\text{ V}, 8\text{ V}]$$


$$\frac{V_o - V_x}{30} = \frac{V_x}{10}$$

$$V_o = 4V_x$$

$$= 8V_1 - 4V_2$$

$$V_1 = 2V_1 - V_2$$

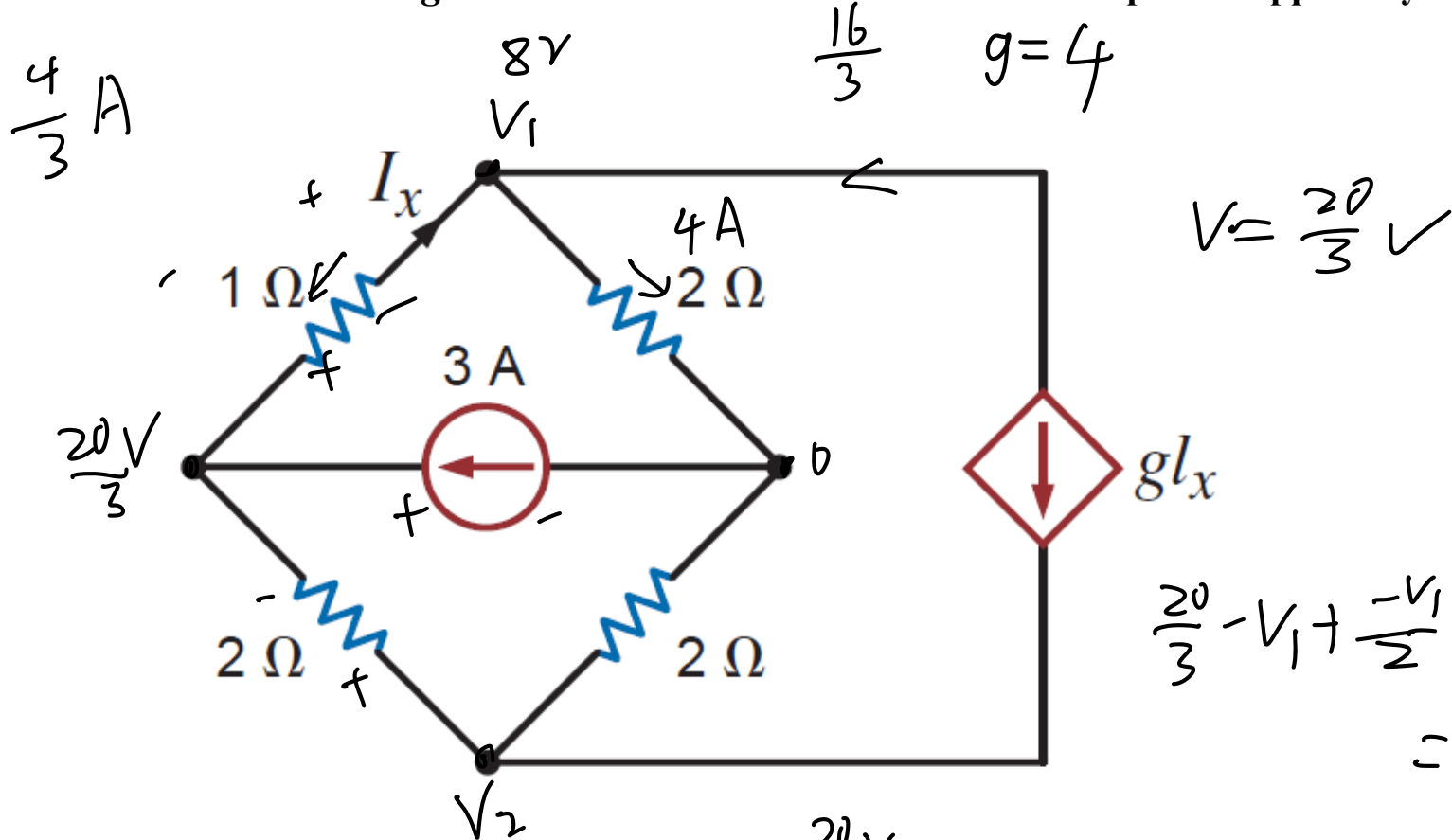Question 5 : Find the value of g in the network shown below such that the power supplied by 3-A source is 20W?




$$\frac{V_2 - \frac{20}{3} V}{2} + 3 = \frac{20}{3} - V_1 \quad \frac{20}{3} - \frac{3}{2}V_1 = 14 - 2V_1 - \frac{10}{3}$$

$$V_2 - \frac{20}{3}V + 6 = \frac{40}{3} - 2V_1 \quad 10 - 14 = -\frac{20}{3}$$

$$V_2 = 14 - 2V_1 \quad V_1 = 8$$

Question 6 : Find V_o in the network using linearity and assume that $V_o = 1V$?

$$\frac{3.4.5}{2.5.5} = 1.8k\Omega$$

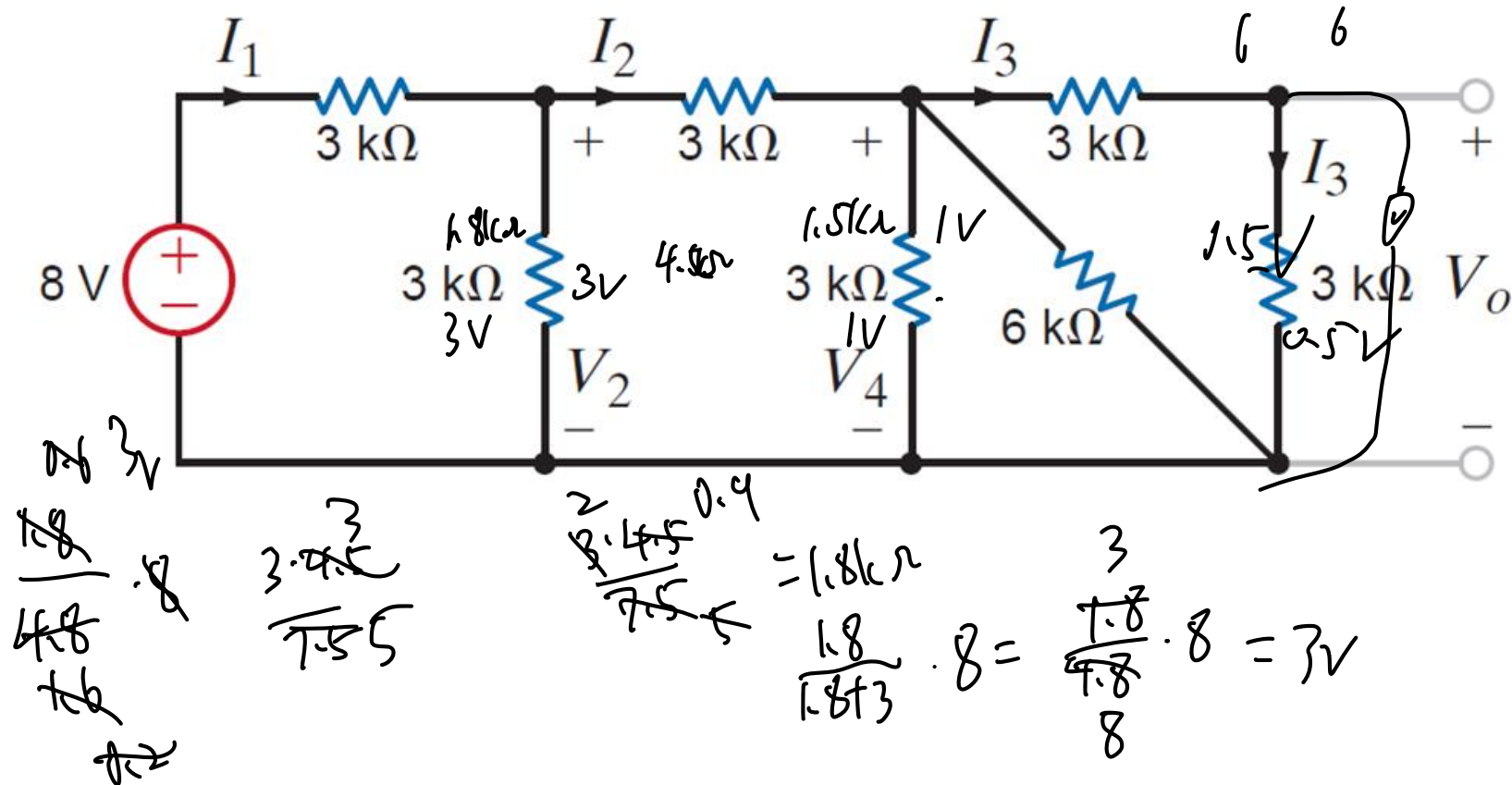

Question 7: Show that circuit can produce the output


$$V_o = K_1 V_1 - K_2 V_2$$

$$\text{only for } 0 \leq K_1 \leq K_2 + 1$$

$$\therefore K_1 = \left(\frac{R_2}{R_1 + R_2} \right) \cdot \left(1 + \frac{R_4}{R_3} \right)$$

$$K_2 = \frac{R_4}{R_3}$$

$$\therefore 0 \leq K_1 \leq K_2 + 1$$

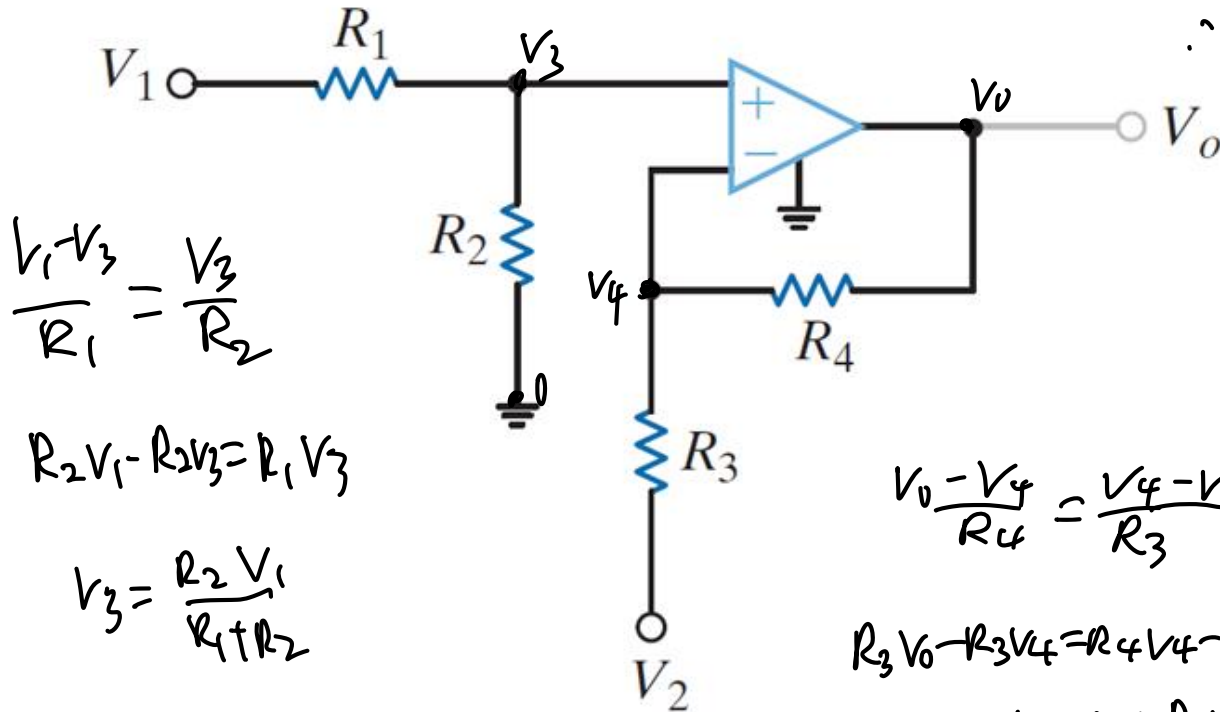

$$\frac{V_1 - V_3}{R_1} = \frac{V_3}{R_2}$$

$$R_2 V_1 - R_2 V_3 = R_1 V_3$$


$$V_3 = \frac{R_2 V_1}{R_1 + R_2}$$

$$\frac{V_o - V_4}{R_4} = \frac{V_4 - V_2}{R_3}$$

$$R_3 V_o - R_3 V_4 = R_4 V_4 - R_4 V_2$$

$$V_o = \left(\frac{R_3 + R_4}{R_3} \right) \cdot \frac{R_2 V_1}{R_1 + R_2} - \frac{R_4 V_2}{R_3}$$

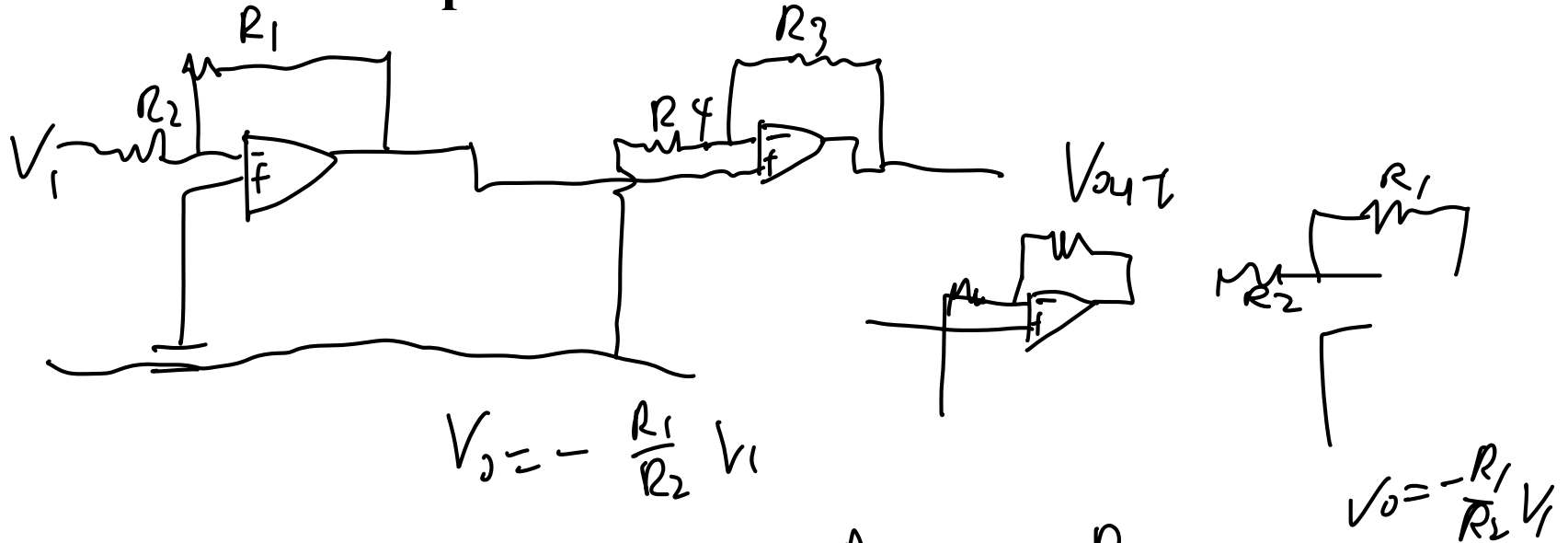Question 8: Design a two stage op-amp network that has a gain of -50,000 while no current into its input terminal. Use no resistors smaller than 1 k Ω



$$V_0 = -\frac{R_1}{R_2} V_i$$

$$V_{out} = \left(1 + \frac{R_3}{R_4}\right) \cdot \left(-\frac{R_1}{R_2}\right) V_i$$

$$\left(1 + \frac{R_3}{R_4}\right) \cdot \left(\frac{R_1}{R_2}\right) = 50000$$

$$\therefore R_3 = R_4 = R_2 = 11k\Omega$$

$$R_1 = 25000k\Omega$$

$$1k\Omega$$