

For C, $I = C \frac{du}{dt}$ $T = R_{Th} C$
 For L, $u = L \frac{di}{dt}$ $T = \frac{L}{R_{Th}}$
 For 一阶恒电源: for C, $v(t) = V(\infty) + (V(0) - V(\infty)) e^{-\frac{t}{T}}$, $i(t) = C \frac{d(v(t))}{dt}$
 ↓
 只含C, L具- for L, $i(t) = I(\infty) + (I(0) - I(\infty)) e^{-\frac{t}{T}}$, $v(t) = L \frac{d(i(t))}{dt}$

For 一阶变电源, Use KCL, KVL 得 ODE

4. 一阶线性方程 形如 $\frac{dy}{dx} = p(x) \cdot y + Q(x)$, 若 $Q(x) = 0$, 则为一阶齐次方程

① $\frac{dy}{dx} = p(x) \cdot y$

$\Rightarrow \frac{dy}{y} = p(x) \cdot dx$, $y = C \cdot e^{\int p(x) dx}$

② $\frac{dy}{dx} = p(x) \cdot y + Q(x)$: 常数变易法

从①出发, 设 $\bar{y} = C(x) \cdot e^{\int p(x) dx}$ 是(1)的一个解

$C'(x) e^{\int p(x) dx} + C(x) \cdot p(x) \cdot e^{\int p(x) dx} = C(x) \cdot p(x) \cdot e^{\int p(x) dx} + Q(x)$

$\Rightarrow Q(x) = C'(x) \cdot e^{\int p(x) dx}$

$\Rightarrow C(x) = \int \frac{Q(x)}{e^{\int p(x) dx}} dx + C$

$y = C \cdot e^{\int p(x) dx} + e^{\int p(x) dx} \cdot \int Q(x) \cdot e^{-\int p(x) dx} dx$
 齐次方程通解 非齐次方程特解

✓ 联立213 解方程!

For 二阶无电源 LC 串联

Solving the differential equation by using initial conditions,

$$s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

A more compact way of expressing the roots is,

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} \quad \text{and} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Source-Free Series RLC Circuit

The characteristic equation can be written as,

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

carries two possible solutions,

$$i_1 = A_1 e^{s_1 t} \quad i_2 = A_2 e^{s_2 t}$$

combining the solution,

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Here, we will discuss 4 possible cases for the solution

$$\frac{\alpha}{\omega_0}$$

For 二阶无电源 LC 并联

Source-Free Parallel RLC Circuit

Solving the differential equation by using initial conditions,

$$s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

A more compact way of expressing the roots is,

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \text{and} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Source-Free Parallel RLC Circuit

The characteristic equation can be written as,

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

carries two possible solutions,

$$v_1 = A_1 e^{s_1 t} \quad v_2 = A_2 e^{s_2 t}$$

combining the solution,

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\frac{1}{2RC}$$

For 二所有恒电源LC串联

Step response to series RLC network

Forms of complete solution

Overdamped

$$v(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Critically damped

$$v(t) = V_s + (A_1 + A_2 t) e^{-\alpha t}$$

Underdamped

$$v(t) = V_s + e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

For 二所有恒电源LC并联

Step response to parallel RLC network

Forms of complete solution

Overdamped

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Critically damped

$$i(t) = I_s + (A_1 + A_2 t) e^{-\alpha t}$$

Underdamped

$$i(t) = I_s + e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

$$\omega_d = \sqrt{\omega^2 - \alpha^2}$$

For 二所有 amp

5.2nd order op-amp circuits
Imp2: Find $v_o(t)$ for $t > 0$ with $v_s = 10 \text{ mV}$, $R_1 = R_2 = 10 \text{ k}\Omega$, $C_1 = 20 \text{ }\mu\text{F}$ and $C_2 = 100 \text{ }\mu\text{F}$

Applying the KCL at node 1,

$$\frac{v_s - v_1}{R_1} = C_1 \frac{dv_1}{dt} + \frac{v_1 - v_o}{R_2}$$

Applying the KCL at node 2,

$$\frac{v_1 - v_o}{R_2} = C_2 \frac{dv_o}{dt}$$

Eliminating v_1 and v_2 from Eq.1-Eq.3 and using the given values for resistors and capacitors, we get

$$\frac{d^2 v_o}{dt^2} + 2 \frac{dv_o}{dt} + 5 v_o = 5 v_s$$

To find the **transient response**, we set $v_s = 0$, the characteristic equation becomes

$$s^2 + 2s + 5 = 0$$

with the roots $s_{1,2} = -1 \pm j2$

The **transient response** will be of the form,

$$v_{ot} = e^{-t} (A \cos 2t + B \sin 2t)$$

The **steady state response** will be of the form,

$$v_{os}(\infty) = v_1(\infty) = v_s$$

The **complete response** will be of the form,

$$v_o(t) = v_{ot} + v_{os}$$


By comparing the values of initial conditions at $v_o(0)$ and $dv_o(0)/dt$, the values of coefficients are

$$A = -10 \quad \text{and} \quad B = -5$$

Thus, the complete solution will be,

$$v_o(t) = 10 - e^{-t} (10 \cos 2t + 5 \sin 2t) \text{ mV}$$

RLC 电路相图:

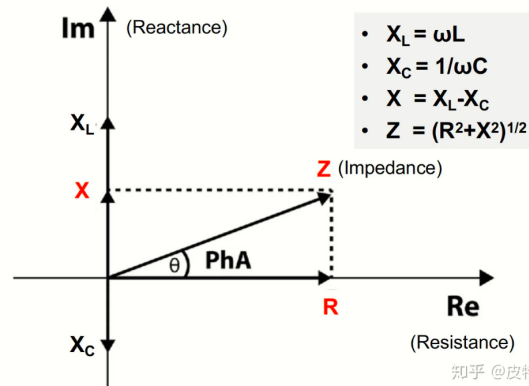

Admittance

- The **admittance Y** is the reciprocal of impedance, measured in siemens (S)

$$Y = \frac{1}{Z} = \frac{I}{V}$$

The admittance can be represented in complex form as

$$Y = G + jB$$

Conductance
 $G = \text{Re}(Y)$

susceptance
 $B = \text{Im}(Y)$

Impedance

- The **impedance Z** of a circuit is the ratio of the phasor voltage **V** to the phasor current **I**, measured in ohms (Ω)
- In the previous lecture, we obtained voltage-current relation for passive elements (**R**, **L** & **C**)

$$\frac{V}{I} = R, \quad \frac{V}{I} = j\omega L, \quad \frac{V}{I} = \frac{1}{j\omega C}$$

So, the phasor form of Ohm's law will be

$$\text{Impedance} = Z = \frac{V}{I}$$

For phasor

Phasors

The complex numbers can also be represented by its polar or exponential form

$$z = r \angle \phi = re^{j\phi}$$

Thus, the complex number in three forms are,


$$z = x + jy \quad \text{Rectangular form}$$

$$z = r \angle \phi \quad \text{Polar form}$$

$$z = re^{j\phi} \quad \text{Exponential form}$$

10

Phasors

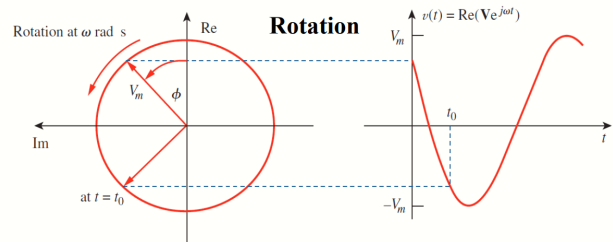

Transformation

$$v(t) = V_m \cos(\omega t + \phi) \quad \Leftrightarrow \quad \mathbf{V} = V_m \angle \phi$$

(Time-domain representation) (Phasor-domain representation)

12

Phasors – Representation

Time Domain

Phasor Domain

$$V_m \cos(\omega t + \phi) \quad \Leftrightarrow \quad V_m \angle \phi$$

$$V_m \sin(\omega t + \phi) \quad \Leftrightarrow \quad V_m \angle \phi - 90^\circ$$

$$I_m \cos(\omega t + \theta) \quad \Leftrightarrow \quad I_m \angle \theta$$


$$I_m \sin(\omega t + \theta) \quad \Leftrightarrow \quad I_m \angle \theta - 90^\circ$$

$$\frac{dv}{dt} \quad \Leftrightarrow \quad j\omega \mathbf{V}$$

$$\int v dt \quad \Leftrightarrow \quad \frac{\mathbf{V}}{j\omega}$$

13

Phasor Representation – Resistor

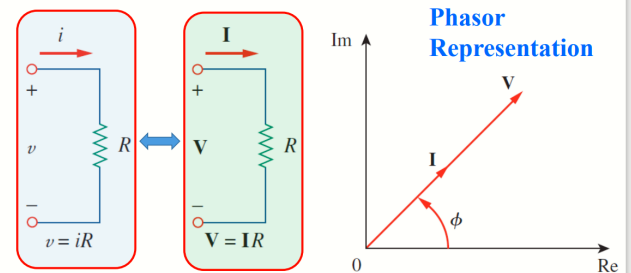


$$v = iR = RI_m \cos(\omega t + \phi)$$

$$\mathbf{V} = RI_m \angle \phi \quad \Rightarrow \quad \mathbf{V} = RI$$

8


Phasor Representation – Capacitor

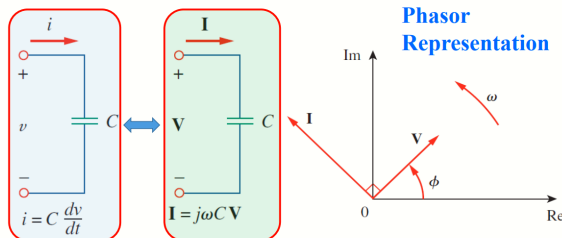

$$i = C \frac{dv}{dt} \quad \Rightarrow \quad \mathbf{I} = j\omega C \mathbf{V}$$

20

Phasor Representation – Inductor

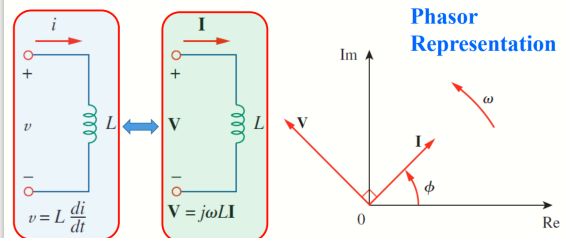

$$v = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \phi) \quad \Rightarrow \quad \mathbf{V} = j\omega L \mathbf{I}$$

19

Phasors – Superposition

The weighted superposition of

$$k_1 f_1(t) + k_2 f_2(t)$$

of co-sinusoids

$$f_1(t) = \text{Re}\{F_1 e^{j\omega t}\} \quad \& \quad f_2(t) = \text{Re}\{F_2 e^{j\omega t}\}$$

with phasor F_1 and F_2 is also a co-sinusoid with a phasor

$$k_1 F_1 + k_2 F_2$$

Phasor Representation – Summary

Voltage – current relationship

Element	Time domain	Frequency domain
R	$v = Ri$	$\mathbf{V} = RI$
L	$v = L \frac{di}{dt}$	$\mathbf{V} = j\omega L \mathbf{I}$
C	$i = C \frac{dv}{dt}$	$\mathbf{V} = \frac{\mathbf{I}}{j\omega C}$

For Average Power and max load power

Instantaneous and Average Power

The phasor form of $i(t) \rightarrow \mathbf{I} = I_m \angle \theta_i$

and $v(t) \rightarrow \mathbf{V} = V_m \angle \theta_v$

The power in the phasor form can be expressed in the form,

$$P = \frac{1}{2} \operatorname{Re}[\mathbf{V}\mathbf{I}^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Maximum Average Power Transfer

- For maximum average power transfer, the load impedance Z_L must be equal to the complex conjugate of the Thevenin impedance Z_{Th}

$$Z_L = R_L + jX_L = R_{Th} - jX_{Th} = Z_{Th}^*$$

~~$$P_{max} = \frac{|V_{Th}|^2}{8R_{Th}}$$~~

For resonance

Resonance : Source – free LC circuit

The co-sinusoids of the signals will be

$$i(t) = \operatorname{Re}\{I e^{j\omega_o t}\} = |I| \cos(\omega_o t + \theta)$$

and,

$$v(t) = \operatorname{Re}\left\{\frac{I}{j\omega_o C} e^{j\omega_o t}\right\} = \frac{|I|}{\omega_o C} \sin(\omega_o t + \theta)$$

are possible with any I and $\theta = \angle I$, and the oscillation frequency will be

$$\omega_o = \frac{1}{\sqrt{LC}}$$

Resonant Frequency

Summary – Resonance

Characteristic	Series circuit	Parallel circuit
Resonant frequency, ω_o	$\frac{1}{\sqrt{LC}}$	$\frac{1}{\sqrt{LC}}$
Quality factor, Q	$\frac{\omega_o L}{R}$ or $\frac{1}{\omega_o RC}$	$\frac{R}{\omega_o L}$ or $\omega_o RC$
Bandwidth, B	$B = \frac{\omega_o R}{L} = \frac{\omega_o}{Q}$	$\frac{\omega_o}{Q}$
Half-power frequencies, ω_1, ω_2	$\omega_o \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_o}{2Q}$	$\omega_o \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_o}{2Q}$
For $Q \geq 10, \omega_1, \omega_2$	$\omega_o \pm \frac{B}{2}$	$\omega_o \pm \frac{B}{2}$

For gain and Transfer function

Decibel Scale

- In communications systems, gain is measured in *bels*
- Historically, the bel is used to measure the ratio of two levels of power or power gain G

$$G = \text{Number of bels} = \log_{10} \frac{P_2}{P_1}$$

- The *decibel* (dB) provides us with a unit of less magnitude. It is 1/10th of a bel and is given by

$$G_{dB} = 10 \log_{10} \frac{P_2}{P_1}$$

Transfer function – Pole and Zero

$$\text{Transfer function} = H(\omega) = \frac{Y(\omega)}{X(\omega)}$$

Zero $\rightarrow H(\omega) = 0, \text{ at } Y(\omega) = 0$

Pole $\rightarrow H(\omega) = \infty, \text{ at } X(\omega) = 0$

For bode plot

$$H(\omega) = \frac{200j\omega}{(j\omega + 2)(j\omega + 10)}$$

12

Bode Plot – Example 1

Solution:

We first put $H(\omega)$ in the **standard form** by dividing out the poles and zeros. Thus,

$$H(\omega) = \frac{10j\omega}{\left(1 + j\frac{\omega}{2}\right)\left(1 + j\frac{\omega}{10}\right)}$$

$$= \frac{10|j\omega|}{\left|1 + j\frac{\omega}{2}\right|\left|1 + j\frac{\omega}{10}\right|} \angle (90^\circ - \tan^{-1}\frac{\omega}{2} - \tan^{-1}\frac{\omega}{10})$$

13

Bode Plot – Example 1

Hence , the magnitude and phase will be,


$$H_{dB} = 20\log_{10}10 + 20\log_{10}|j\omega| - 20\log_{10}\left|1 + \frac{j\omega}{2}\right| - 20\log_{10}\left|1 + \frac{j\omega}{10}\right|$$

$$\phi = 90^\circ - \tan^{-1}\frac{\omega}{2} - \tan^{-1}\frac{\omega}{10}$$

14

Bode Plot – Example 1


$$H_{dB} = 20\log_{10}10 + 20\log_{10}|j\omega| - 20\log_{10}\left|1 + \frac{j\omega}{2}\right| - 20\log_{10}\left|1 + \frac{j\omega}{10}\right|$$

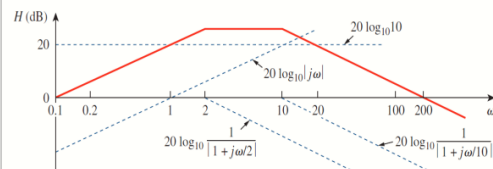

15

Bode Plot – Example 1
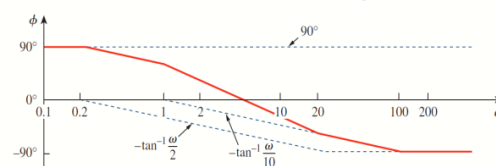
$$\phi = 90^\circ - \tan^{-1}\frac{\omega}{2} - \tan^{-1}\frac{\omega}{10}$$



16