



ANALOG SIGNAL PROCESSING



ECE 210 & 211

Exercise 2

30th March, 2023

Prof. Yang Xu (徐杨)

yangxu-isee@zju.edu.cn

Yue Dai, yuedai@zju.edu.cn

Jinfeng Huang, huangjinfeng@zju.edu.cn

Yance Chen, 12031045@zju.edu.cn

Yuan Ma, 22241064@zju.edu.cn

Youshui He, 22241003@zju.edu.cn

Zongwen Li, zongwen_li@zju.edu.cn

Muhammad Malik, mmalik@zju.edu.cn

Munir Ali, Munir_li@zju.edu.cn

Muhammad Abid, abid_anwar@zju.edu.cn



ZJU-UIUC Institute

Zhejiang University / University of Illinois at Urbana-Champaign Institute



Question 1:

$$\frac{dV}{dt} = P(t) \cdot V + Q(t)$$

$$V(t)_o = e^{\int -P(t) dt}$$

$$V(t)_p = e^{\int P(t) dt} \int Q(t) e^{\int -P(s) ds} dt$$

Let us find R_L for maximum power transfer and the maximum power transferred to this load in the circuit below.

when the load is open.

$$4 \times 10^3 \cdot (4 - I_x) + 2 \times 10^3 I_x = 2 \times 10^3 I_x$$

$$\Rightarrow I_x = 4 \text{ mA}$$



$$\begin{cases} V_{out} = 8 \text{ V} \\ I = 0 \end{cases}$$

when the load is short


$$(4 - \frac{3}{2} I_x) \cdot 4 + 2 I_x = 2 I_x$$

$$4 = \frac{3}{2} I_x \quad I_x = \frac{8}{3} \text{ mA}$$
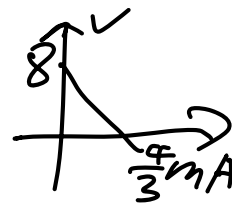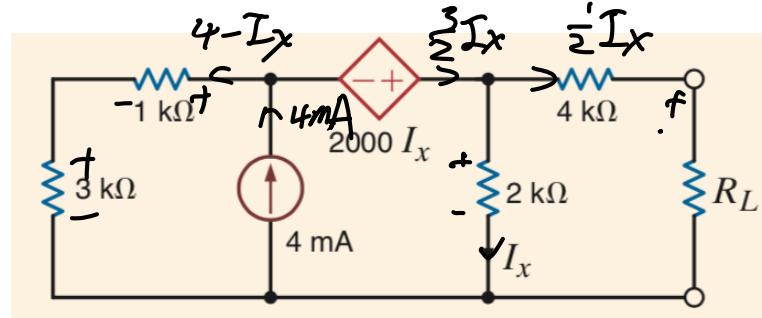
$$\Rightarrow \begin{cases} V_{out} = 0 \\ I_{out} = \frac{4}{3} \text{ mA} \end{cases}$$



$$R_L = 6 \text{ k}\Omega$$

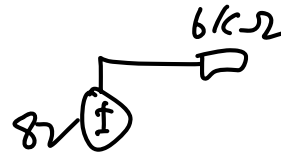

$$R = \frac{8 \times 2}{2 + 3} = 6$$

$$P = \frac{16}{6} = \frac{8}{3} \text{ mW}$$

Question 2 : The circuit is in steady state prior to time $t=0$, when the switch is closed. Calculate the current $i(t)$ for $t > 0$?

when $t < 0$

$$i(t) = \frac{36 - 12}{12} A = 2 A, \quad u(t) = 36 - 2 \times 2 = 32 V$$

when $t \geq 0$

$$\lim_{t \rightarrow \infty} u(t) = 36 \cdot \frac{6}{6+2} V = 27 V$$


$$\therefore T = R_{Th}C = \frac{12}{8} \cdot 1 \times 10^{-4} \times 10^3 = 0.15 s$$

$$u(t) = 27 + (32 - 27) \cdot e^{-\frac{20}{3}t} = 27 + 5e^{-\frac{20}{3}t}$$

$$I_2 = \frac{36 - 27 - 5e^{-\frac{20}{3}t}}{2}$$

$$= 4.5 - 2.5e^{-\frac{20}{3}t} \text{ mA}$$
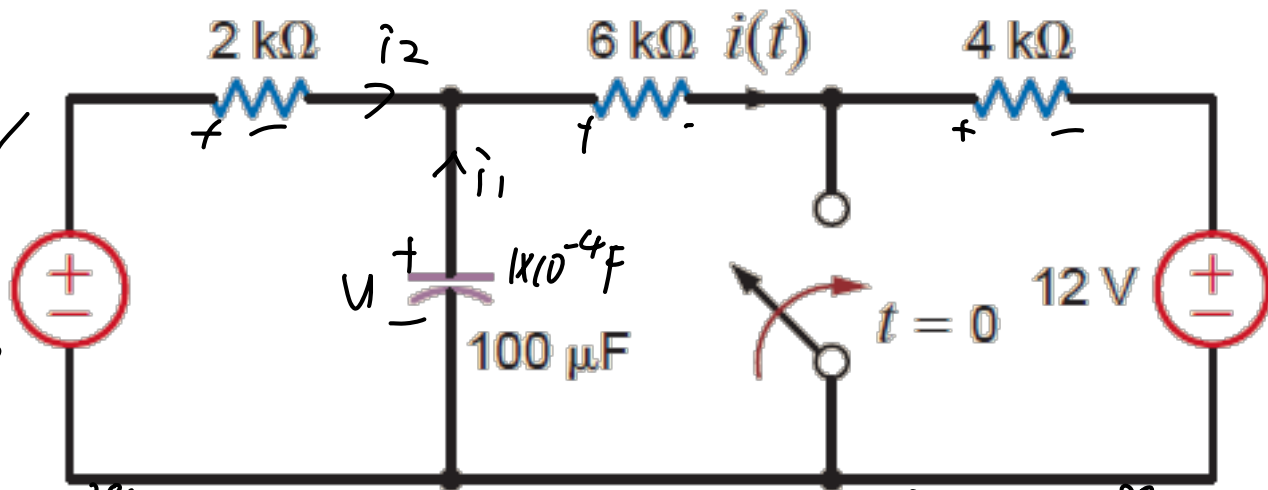
$$\therefore i(t) = i_1 + i_2 = 4.5 - 2.5e^{-\frac{20}{3}t} + \frac{10}{3}e^{-\frac{20}{3}t}$$



$$\frac{36}{8}$$




Question 3: Find $i(t)$ for $t > 0$?

Note: The switch position is changed at $t = 0$

$$= 4.5 t_6^5 e^{-\frac{20}{6}t}$$
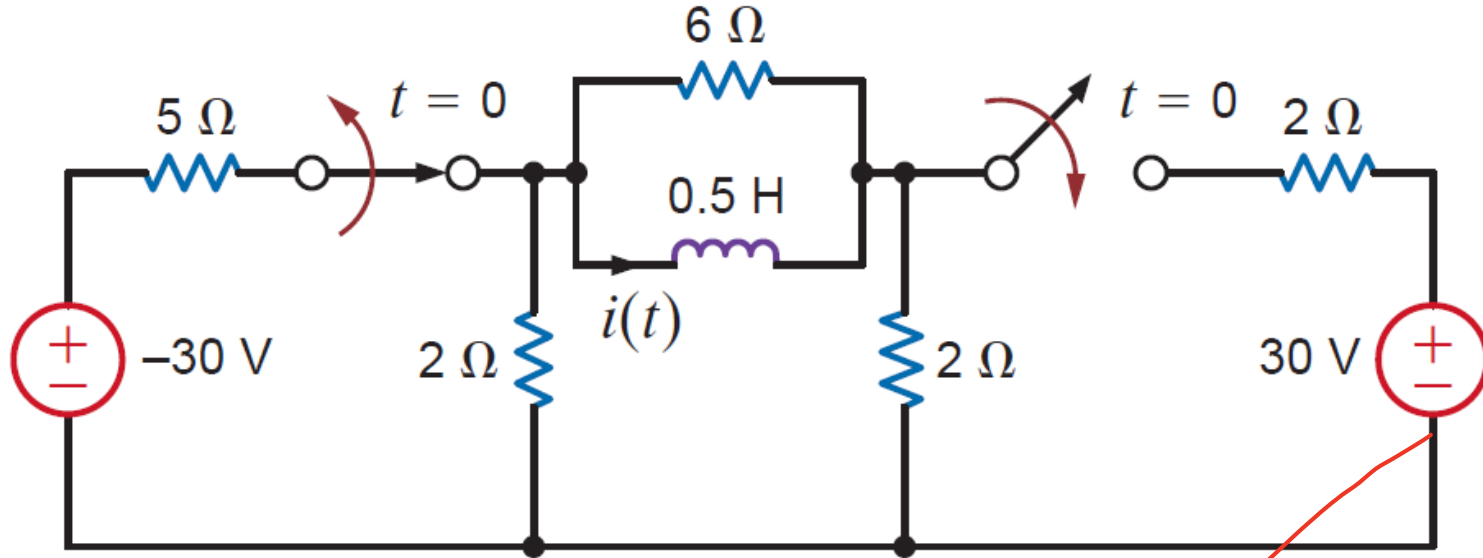
$$\frac{5}{2} \quad \frac{15}{6} \quad \frac{20}{6}$$



for $t < 0$

$$i(t) = -\frac{30 \cdot \frac{1}{1.5}}{2} = -2.5 \text{ A}$$

for $t \geq 0$

$$R_{Th} = \frac{18}{9} \Omega = 2 \Omega, T = \frac{L}{R} = \frac{0.5}{2} = 0.25 \text{ s}$$

$$i(\infty) = \frac{30V}{2} = -5 \text{ A}$$

$$\therefore i(t) = -5 + (-2.5 + 5)e^{-4t} = -5 + 2.5e^{-4t} \text{ A}$$

Question 4:

Let $R = 1 \Omega$, $C = 1F$, and

$$\int u dv = uv - \int v du \quad du = -\sin t dt$$

$$u = \cos t, \quad dv = e^t dt \quad v = e^t \quad v_s(t) = \cos(t) \quad w = 1$$

in the RC circuit shown earlier in Figure . Then, for $t > 0$, the capacitor voltage $v(t)$ will be the solution to the ODE

$$\begin{aligned} \int \cos t e^t dt &= \cos t e^t + \int e^t \sin t dt \\ &= \cos t e^t + e^t \sin t - \int e^t \cos t dt \end{aligned}$$

$$\frac{dv}{dt} + v(t) = \cos(t).$$

Determine $v(t)$ for $t > 0$, assuming zero initial state—that is, $v(0^-) = 0$.


$$\frac{dv}{dt} = -v(t) + \cos(t)$$

$$\therefore V(t) = ce^{\int -1 dt} = ce^{-t}$$

$$V(t)_p = e^{\int -1 dt} \int \cos s e^{\int 1 ds} ds$$

$$= e^{-t} \int \cos s e^s ds$$
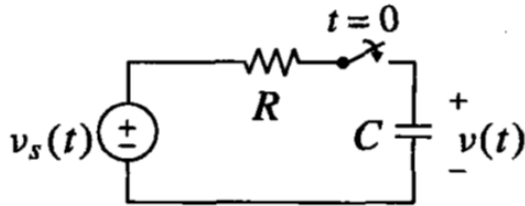
$$= e^{-t} \frac{1}{2} (\cos t e^t + \sin t e^t) = \frac{1}{2} \cos t + \frac{1}{2} \sin t$$



$$\therefore V(t) = ce^{-t} + \frac{1}{2} \cos t + \frac{1}{2} \sin t$$





$$\text{For } C \quad v(0) = V(0) = c + \frac{1}{2} = 0 \Rightarrow c = -\frac{1}{2}$$

Question 5:

The capacitor is initially discharged.

(a) The waveform in Fig.1(b) is applied at the input of the differentiator circuit shown in Fig.1(a). If $R = 1K$, and $C = 2\mu F$, determine the waveform at the output of the op-amp. **output**

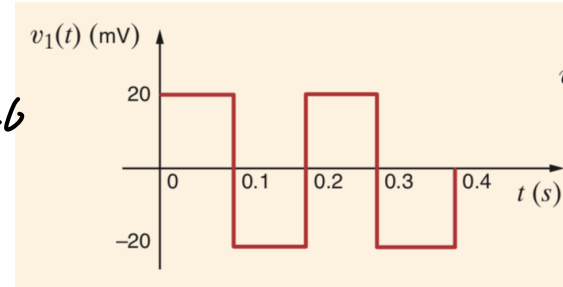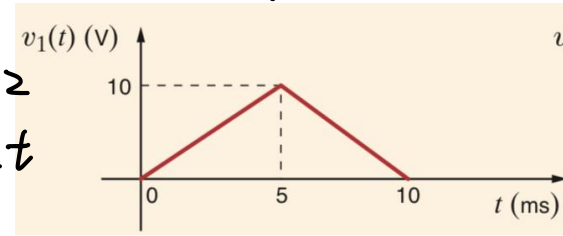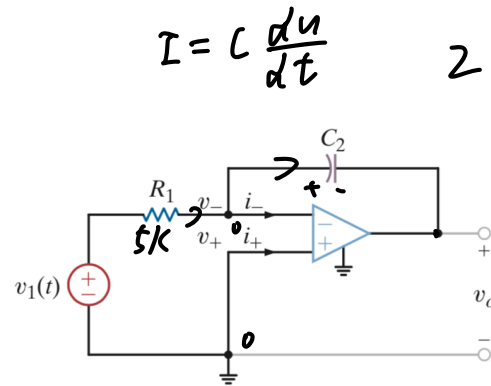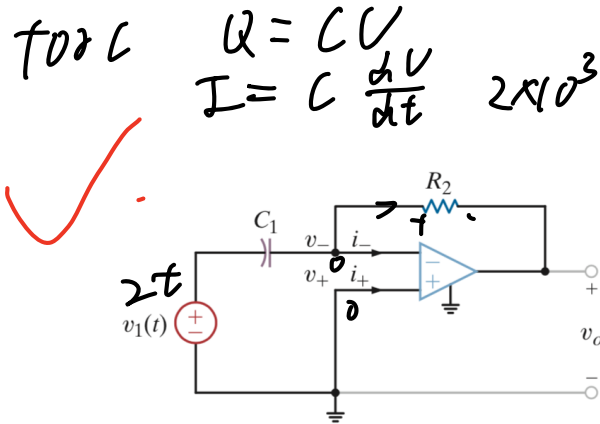(b) If the integrator shown in Fig.2(b) has the parameters $R_1 = 5K$ and $C_2 = 0.2\mu F$, determine the waveform at the op-amp output if the input waveform is given as in Fig.2(a).



$$\therefore V(t) = -\frac{1}{2} e^{-t} + \frac{1}{2} \cos t + \frac{1}{2} \sin t$$

2×10^3
 $2 \times 10^3 \times 2 \times 10^{-6} = 4 \times 10^{-3}$
 $4V$

$\frac{20}{5} \times 10^{-6} = 4 \times 10^{-6} \quad 2 \times 10^{-6}$
 $V_0 = 0 - V_2$

$\frac{dV}{dt} = 2$
 $V = 2t$

Question 6: A Variable frequency source having amplitude 6V connected to a series RL circuit of values $L=40\text{mH}$ and $R= 80 \text{ ohms}$.


a) At what frequency , does $V_R = V_L$?

b) What would be the phase angle ϕ at that frequency?

c) What will be the current amplitude and RMS value?

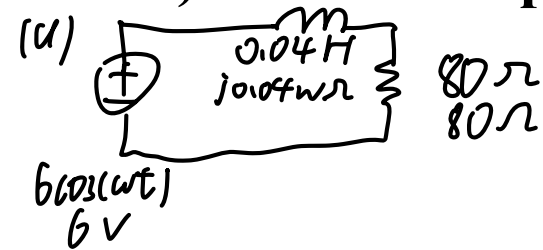d) Write an expression for current at steady state in phasor form?

$I = \frac{Ae^{-t}}{B \cos t + C \sin t}$



$$6 \cdot \frac{|j0.04\omega|}{|80 + j0.04\omega|} = 6 \cdot \frac{180}{180 + j0.04\omega}$$

$$\Rightarrow 0.04\omega = 80 \Rightarrow \omega = 2000$$

$$\Rightarrow f = \frac{2000}{2\pi} = 318.3 \text{ Hz}$$

$$(b) \phi = \arctan\left(\frac{V_L}{V_R}\right) = 45^\circ$$

$$(c) I = \frac{6}{80 + j80} \therefore |I| = \frac{6}{80\sqrt{2}} = \frac{3\sqrt{2}}{80} \text{ A} = I_{\text{max}}$$

$$\text{RMS value} = |I| \cdot \frac{1}{\sqrt{2}} = \frac{3}{80} \text{ A}$$


$$(d) I = \text{Re}\{ |I| e^{j\omega t} \} = \frac{3\sqrt{2}}{80} \cos \omega t$$

$$\text{phasor form: } \frac{6}{80 + j80}$$

$$= \frac{2}{2\pi} = 318.1/2$$

Question 7: Find $v_1(t)$ in the network using phasor method?

$$\omega = 4$$

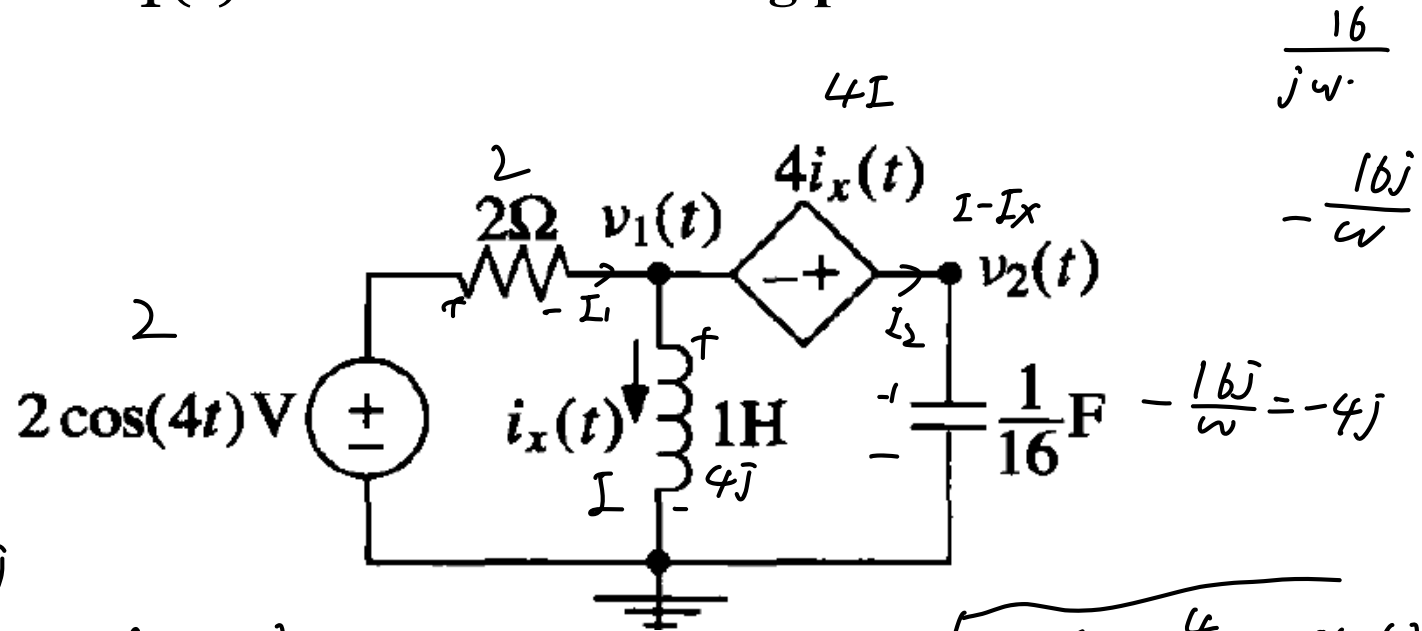

$$2 = 2I + I_x 4j$$

$$I_x \cdot 4j + 4I_x = -4j \cdot (I - I_x) \\ = -4jI + 4jI_x$$

$$1 = I + 2I_x j = jI_x + 2jI_x = 3jI_x \quad I_x = -\frac{1}{3}j$$

$$I_x = -jI \Rightarrow I = jI_x \quad \therefore v_1 = 0 + 4j \left(-\frac{1}{3}j\right) = \frac{4}{3} V$$

$$\underline{v_1(t) = \frac{4}{3} \cos(4t)}$$

Question 8:

Let us determine the phasor diagram for the series circuit shown below.

$$\text{let } \omega = 377 \text{ rad/s}$$

$$Z = 4 + j\omega L + \frac{1}{j\omega C}$$

$$= 4 + 6j + \frac{2}{j}$$

$$= 4 + 6j - 2j = 4 + 4j$$

$$\therefore I = \frac{V_s}{Z} =$$

assume use I as base line

$$\therefore V_R = 4I = 4I$$


$$V_L = 6jI = 6I \angle 90^\circ$$

$$V_C = -2jI = 2I \angle -90^\circ$$


$$V_s = 4\sqrt{2}I \angle 45^\circ$$

Tips: assume $\omega = 377 \text{ rad/s}$, then $\omega L = 6$, $\frac{1}{\omega C} = 2$

$$\phi = \arctan\left(\frac{|V_L| - |V_C|}{|V_R|}\right) = \arctan 1 = 45^\circ$$

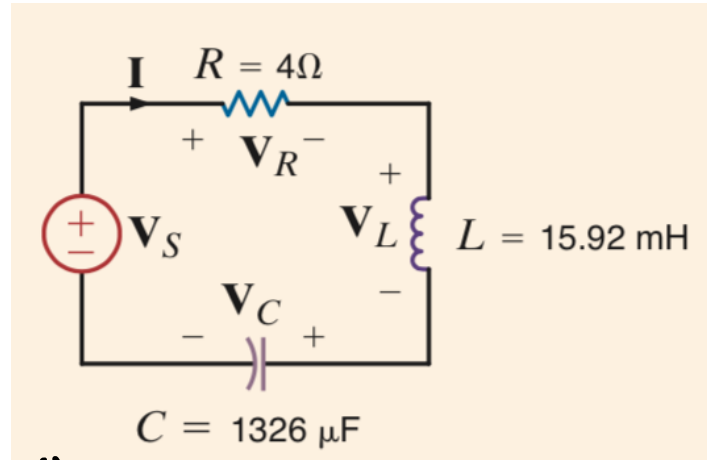

\therefore phasor

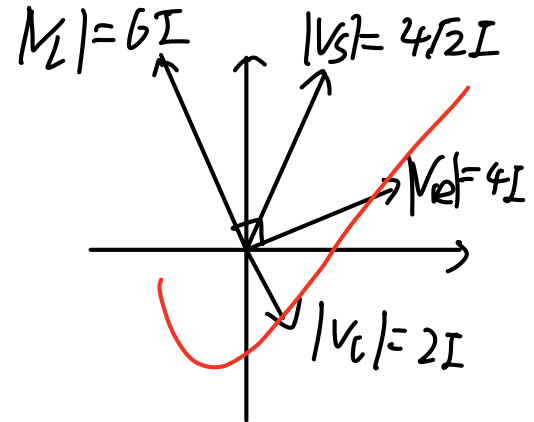

Question 9:


Let us determine the current \mathbf{I}_0 in the network below using nodal analysis, loop analysis, superposition, source exchange, Thévenin's theorem, and Norton's theorem.

$$I_1 = \frac{V_1}{1+j}$$

$$V_2 = V_1 + 6V \Rightarrow V_1 = V_2 - 6 = I_0 - 6$$

$$I_0 = \frac{V_2}{1\Omega}$$

$$I_2 = \frac{V_2}{1-j} A$$

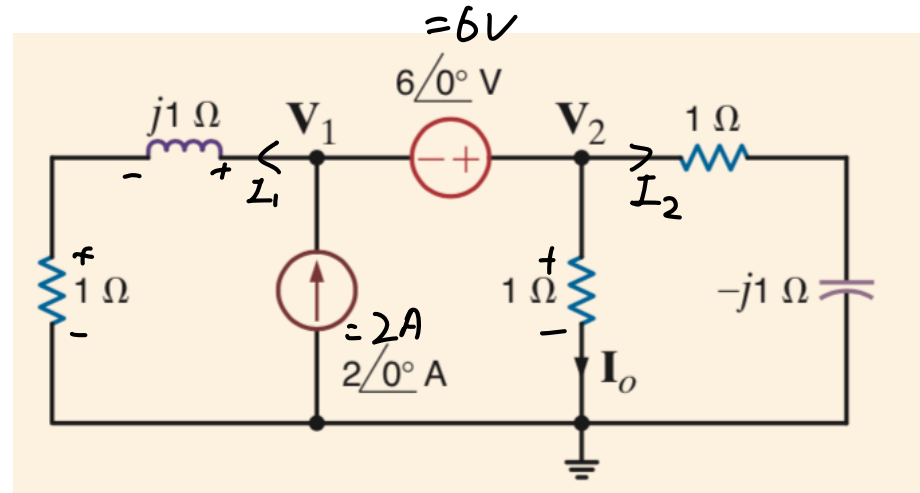

$$I_0 = \frac{5}{2} - \frac{3}{2}j$$

$$2 = I_1 + I_2 + I_0 = \frac{I_0 - 6}{1+j} + \frac{I_0}{1-j} + I_0$$

$$2 = \frac{(I_0 - 6)(1-j)}{2} + \frac{I_0(1+j)}{2} + I_0 = 2I_0 + 3j - 3$$

$$I_0 = \frac{5}{2} - \frac{3}{2}j$$

$$2I_0 = 5 - 3j$$

$$\frac{I_0 - 6 = \cancel{I_0 j} + 6j + I_0 + \cancel{I_0 j} + 2I_0}{2} = \frac{4I_0 + 6j - 6}{2} = 2I_0 + 3j - 3$$