

### Question 1:

Determine the power of each current sources and voltage sources in the following circuit in Figure 1.

assume  $V_a = 0$

use KCL at d, c, a, b

$$i_1 + 5 + 1 = 0$$

$$3i_3 + 2 = 1$$

$$1 + i_2 + 3i_1 + 5 = 0$$

$$1 + i_2 = i_3 + 2$$

$$\Rightarrow \begin{cases} i_1 = -6A \\ i_3 = -4A \\ i_2 = -3A \end{cases}$$

∴ for voltage sources:

$$P_1 = -8 \cdot 6 \text{ W} = -48 \text{ W}$$

$$P_2 = 12 \cdot 3 \text{ W} = 36 \text{ W}$$

$$P_3 = -4 \cdot 10 \text{ W} = -40 \text{ W}$$

$$\Rightarrow \begin{cases} P_4 = -10 \cdot 5 \text{ W} = -50 \text{ W} \\ P_5 = -24 \cdot 1 \text{ W} = -24 \text{ W} \\ P_6 = -22 \cdot 3 \text{ W} = -66 \text{ W} \\ P_7 = 12 \cdot 1 \text{ W} = 12 \text{ W} \\ P_8 = 2 \cdot 2 \text{ W} = 4 \text{ W} \end{cases}$$

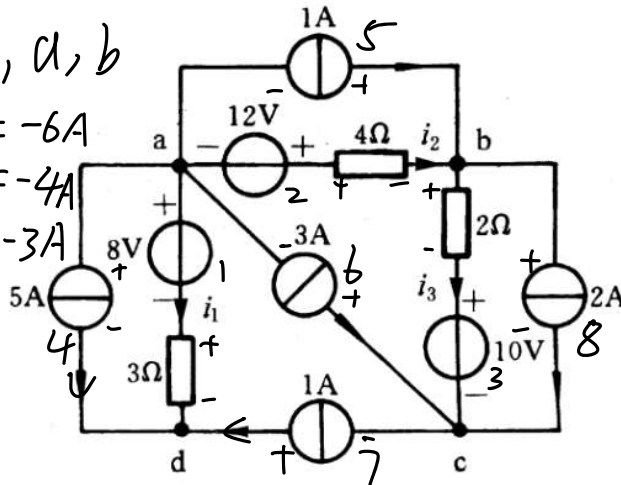


Figure 1

$$V_7 = -22 - 8 + 18$$

Use KVL

$$V_4 = 8 + 3i_1$$

$$V_5 + i_2 \cdot 4 = 12$$

$$V_6 + 10 + 2i_3 + i_2 \cdot 4 = 12$$

$$V_6 + V_7 + 3i_1 + 8 = 0$$

$$V_8 = 2i_3 + 10$$

$$\Rightarrow \begin{cases} V_4 = -10 \text{ V} \\ V_5 = 24 \text{ V} \\ V_6 = 22 \text{ V} \\ V_7 = -12 \text{ V} \\ V_8 = 2 \text{ V} \end{cases}$$

## Question 2:

In the following circuit in Figure 2,  $R_L$  is an adjustable resistor. The  $R_L$  can get maximum power of  $P_{\max} = 4.5 \text{ W}$  when  $R_L$  equals to  $2 \Omega$ . Determine  $R$  and  $U_S$  in the circuit.

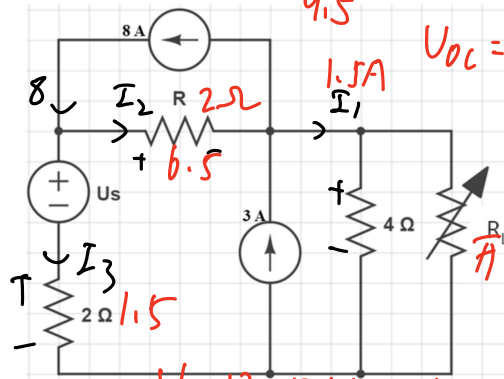


Figure 2

when open :

$$\begin{cases} I_2 + I_3 = 8 \\ I_2 - I_1 = 5 \\ U_S + 2I_3 = RI_2 + 4I_1 \end{cases} \quad \begin{cases} 5 - I_1 + I_3 = 8 \\ I_3 = 3 - I_1 \end{cases}$$

$$\Rightarrow U_S + 6 - 2I_1 = 5R + RI_1 + 4I_1$$

$$\Rightarrow U_S + 6 - 5R = (6 + R)I_1 \Rightarrow I_1 = \frac{U_S + 6 - 5R}{6 + R}$$

$$\Rightarrow U_{out} = 4I_1 = \frac{4U_S + 24 - 20R}{6 + R}$$

when short :

$$\begin{cases} I_2 + I_3 = 8 \\ I_2 - I_1 = 5 \\ U_S + 2I_3 = RI_2 \end{cases} \quad \begin{cases} I_3 = 3 - I_1 \\ I_2 = 5 + I_1 \end{cases}$$

$$\Rightarrow U_S + 6 - 2I_1 = 5R + RI_1$$

$$\Rightarrow I_1 = \frac{U_S + 6 - 5R}{2 + R}$$

$$\Rightarrow U_{out} = 0$$

$$I_{out} = \frac{U_S + 6 - 5R}{2 + R}$$

$$\therefore R_{equal} = \frac{U_{out}}{I_{out}}$$

$$= \frac{4U_S + 24 - 20R}{6 + R} \cdot \frac{2 + R}{U_S + 6 - 5R} = 2$$

$$P_{\max} = \frac{1}{2} \cdot U_{out} I_{out} = \frac{1}{2} \cdot \frac{4U_S + 24 - 20R}{6 + R} \cdot \frac{U_S + 6 - 5R}{2 + R} = 4.5$$

$$(U_S - 4)^2 = 8 \cdot 9$$

$$\begin{aligned} 8(U_S - 4) &= \pm 3 \cdot 2\sqrt{2} \\ (4U_S + 6)(U_S - 4) &= 4.5 \\ \frac{4U_S + 6}{16} &= 4.5 \end{aligned} \quad \begin{aligned} U_S - 4 &= \pm 3\sqrt{2} \\ U_S &= 4 \pm 6\sqrt{2} \end{aligned}$$

$$8U_S + 48 - 40R + 4U_S R + 24R - 20R^2 = 12U_S + 72 - 60R + 2RU_S + 12R - 10R^2$$

$$4U_S + 24 - 20R - 2U_S R - 12R + 10R^2 = 0$$

$$4U_S^2 + 24U_S - 20RU_S + 24U_S + 144 - 120R - 20U_S R - 120R + 100R^2 = 108 + 72R + 4R^2$$


$$4V_s^2 + 48V_s - 40RV_s + 36 - 312R + 91R^2 = 0$$

### Question 3:

Design an op-amp circuit that performs the following operation

$$v_0 = 3v_1 - 2v_2$$

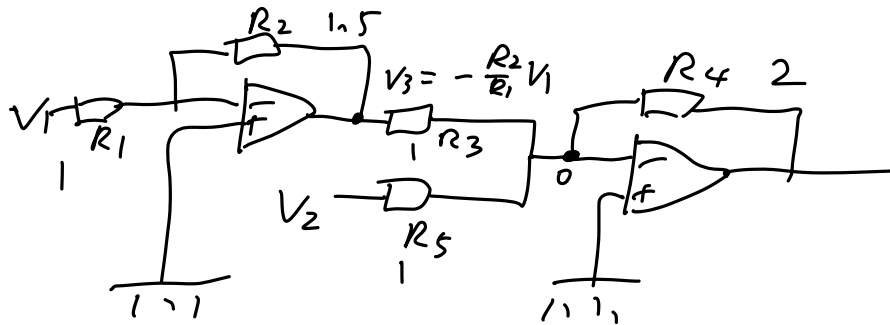All resistances must  $\leq 100\text{k}\Omega$



$$- \frac{R_4}{R_3} \cdot \left( - \frac{R_2}{R_1} \right) V_1 = \frac{R_4 R_2}{R_3 R_1} V_1 = 3 V_1$$

$$- \frac{R_4}{R_5} \cdot V_2 = -2 V_2$$

$$R_4 = 2 \text{ k}\Omega$$


$$R_5 = 1 \text{ k}\Omega$$

$$R_2 = 1.5 \text{ k}\Omega$$

$$R_1 = R_3 = 1 \text{ k}\Omega$$
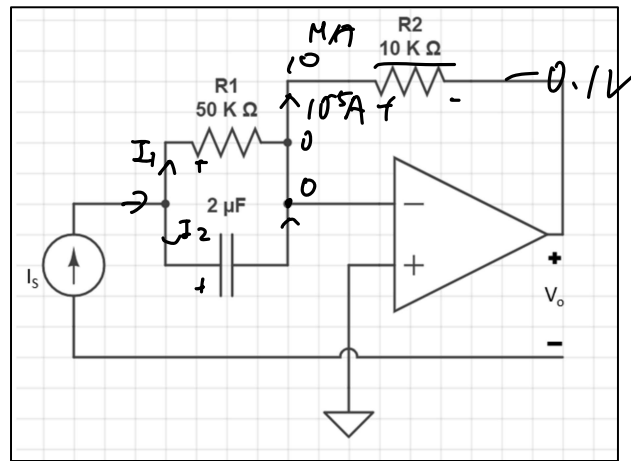
#### Question 4:

Determine  $v_o(t)$  for  $t > 0$  in Figure 4. Let  $i_s = 10u(t) \mu A$ , and assume that capacitor is initially uncharged?



$$V_0 = -10^{-5} \cdot 10^4 = -0.1V$$

$$Q = CV$$

$$I = C \frac{dV}{dt}$$

$$V = 50k I_1$$

Figure 4

$$\begin{cases} I_2 = I_s - I_1 \end{cases}$$

$$\begin{cases} I_2 = C \frac{50k dI_1}{dt} = 2 \times 10^{-6} \cdot 5 \times 10^4 \end{cases}$$

$$5 \times 10^{-4}$$

$$\begin{aligned} \therefore 0.1 I_1' &= I_s - I_1 \Rightarrow I_1' = -10 I_1 + 10 I_s \\ &= -10 I_1 + 10^{-4} u(t) \\ &= -10 I_1 + 10^{-4} \end{aligned}$$

$$10^{-5}$$

$$\therefore I_1(t)_0 = C e^{\int -10 dt} = C e^{-10t}$$

$$\therefore V_V \approx 0.5(1 - e^{-10t})V$$

$$\begin{aligned} I_1(t)_p &= e^{\int -10 dt} \cdot \int 10^{-4} e^{10t} dt \\ &= e^{-10t} \cdot \frac{10^{-4}}{10} e^{10t} = 10^{-5} \end{aligned}$$

$$\therefore I_1(t) = C e^{-10t} + 10^{-5}$$

$$I_1(0) = 0 \Rightarrow C = -10^{-5}$$

$$\therefore I_1(t) = 10^{-5}(1 - e^{-10t})$$

## Question 5:

5.1 In Figure 5(a),

- Determine the equivalent impedance of the network if the frequency  $f=60$  Hz.
- Compute the current  $i(t)$  if the voltage source is  $v(t) = 50\cos(\omega t + 30^\circ)$ .
- Calculate the equivalent impedance if the frequency  $f=400$  Hz.

5.2 Sketch the phasor diagram for the network shown in Figure 5(b)

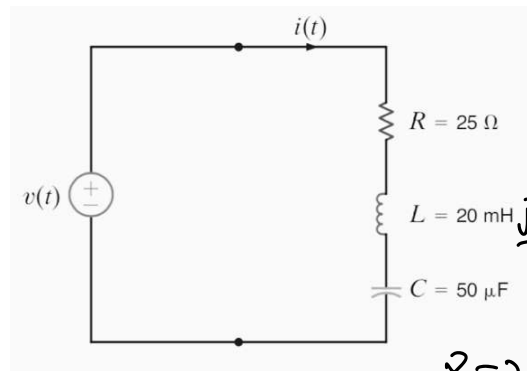


Figure 5(a)


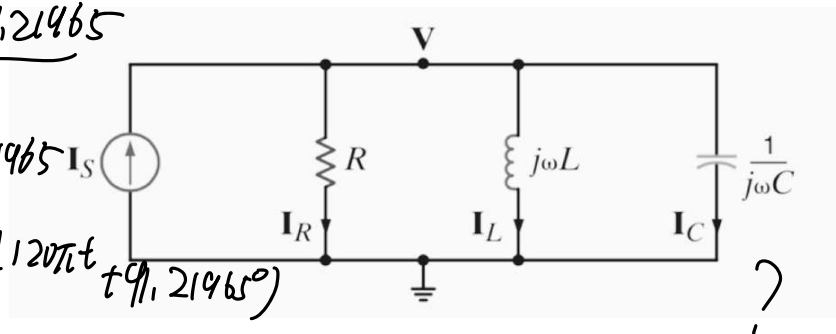


Figure 5(b)

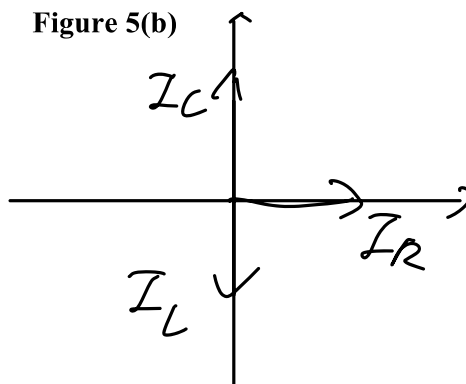

$$\begin{aligned}
 (b) &: 50 \angle 30^\circ (120\pi t + \frac{\pi}{6}) \\
 &= 50 \angle 30^\circ \\
 &= 25 + 2.4j - \frac{500}{3\pi}j \\
 &\approx \frac{50 \angle 30^\circ}{25 - 45.5118j} \\
 &= \frac{50 \angle 30^\circ}{51.9261 \angle -61.21965^\circ}
 \end{aligned}$$

$$= 0.9624 \angle 91.21965^\circ I_s$$

$$\therefore i(t) = 0.9624 \cos(120\pi t + 91.21965^\circ)$$

for  $V$

for  $V$

$j\omega L$

$j \cdot 0.02 \cdot 400$

$2\pi \cdot 60$

(a)

(c)

$f = 60 \text{ Hz} \Rightarrow \omega = 120\pi$

$\omega = 800\pi$

$25\Omega$

$25\Omega$

$j\omega L = 2.4\pi j\Omega$

$16j\pi$

$= \frac{1}{j\omega C} = \frac{500}{3\pi j}\Omega$

$\frac{25}{\pi j}$


$Z = 25 + 2.4\pi j + \frac{500}{3\pi j}$

(b)

$$\frac{(-4-28j)(6+8j)}{25} = \frac{-8j-42}{25}$$

Question 6:

In Figure 6,

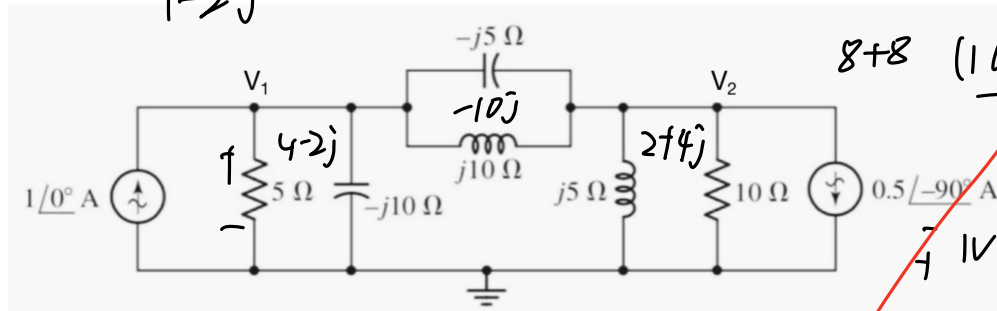a) Find the time-domain node voltages  $v_1(t)$  and  $v_2(t)$ .b) Use superposition to find  $V_1$ .

(a) use KCL for node 1 Figure 6

$$1\angle 0^\circ = \frac{V_1}{5} + \frac{V_1}{-10j} + \frac{V_1 - V_2}{-5j} + \frac{V_1 - V_2}{10j} = 1 = \frac{2V_1j - 2V_1 + V_2}{10j}$$

$$-0.5\angle -90^\circ = \frac{V_2}{10} + \frac{V_2}{5j} + \frac{V_2 - V_1}{-5j} + \frac{V_2 - V_1}{10j} = 0.5j = \frac{V_2j + 2V_2 + 2V_1 - 2V_2 + V_2 - V_1}{10j}$$

$$\therefore 10j = 2V_1j - 2V_1 + V_2$$

$$5j = V_2j + V_1 + V_2$$

$$V_1 = \frac{10j - V_2}{2j - 2}$$

$$-5 = V_2j + \frac{10j - V_2}{2j - 2} + V_2$$

$$10 - 10j = -2V_2 - 2V_2j + 10j - V_2 + 2V_2j - 2V_2$$

$$10 - 20j = -5V_2$$

$$V_2 = -2 + 4j$$

$$\frac{(2+6j)(2j+2)}{-8} = \frac{-8+16j}{-8} = 1-2j$$

for left source

$$\frac{(4-12j)(2+4j)}{6-8j} = \frac{(56-8j)(6+8j)}{100} = \frac{400+400j}{100} = 4+4j$$

$$\frac{2+4j}{6-8j} \cdot 4-2j \cdot (-0.5j)$$

$$\frac{8+8}{100} (16+12j)(6+8j) \cdot (-0.5j)$$

$$2j \quad 1$$

$$\frac{24j - 24 + 24j - 24}{10j}$$

$$= \frac{V_2j + V_1 + V_2}{10j}$$

### Question 7:

- (a) Apply source transformation to find  $v_x$  in the circuit of Figure 1(a).  
 (b) In the circuit of Figure 7(b) find  $i(t)$  for  $t > 0$ .

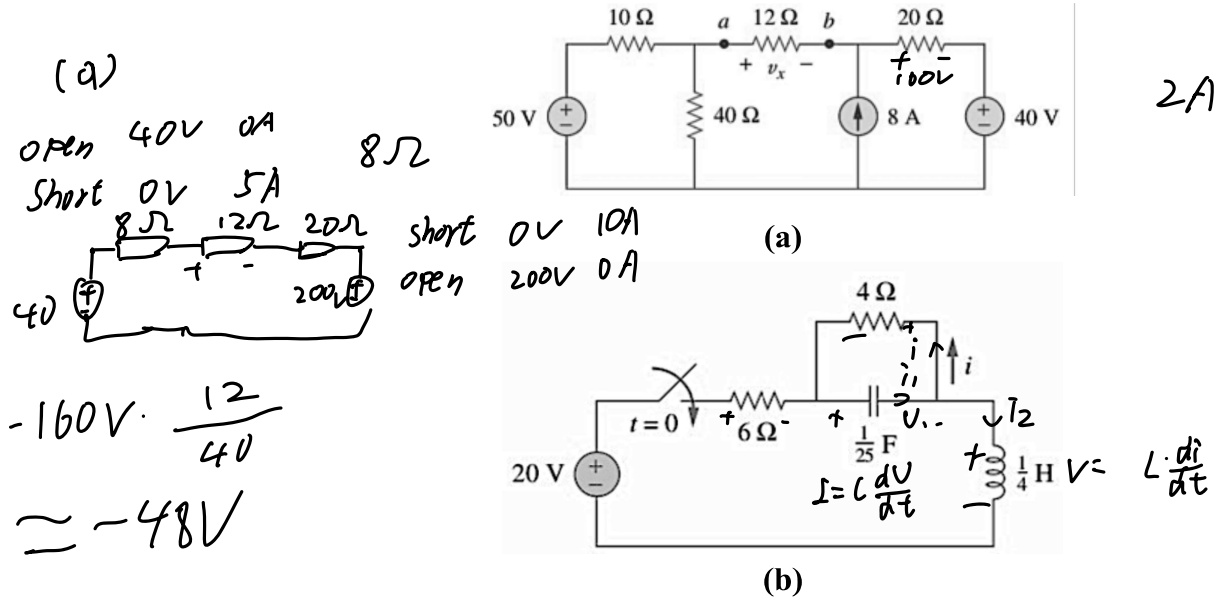


Figure 7

(b) KVL:  $20 = 6i_2 + V + L \frac{di_2}{dt}$

$V = -4i$

KCL:  $i = C \frac{dV}{dt} - i_2 \quad i = -\frac{1}{4}V$

$i_2 = -i + C \frac{dV}{dt} = \frac{1}{4}V + C \frac{dV}{dt}$

$\frac{di_2}{dt} = \frac{1}{4} \frac{dV}{dt} + C \frac{d^2V}{dt^2}$

$20 = \frac{3}{2}V + 6C \frac{dV}{dt} + V + LC \frac{d^2V}{dt^2} + \frac{1}{16} \frac{dV}{dt}$

$\Rightarrow 0.01 \frac{d^2V}{dt^2} + \frac{121}{400} \frac{dV}{dt} + \frac{5}{2}V = 20$

$0.01x^2 + \frac{121}{400}x + \frac{5}{2} = 0$

$x^2 + \frac{121}{4}x + 250 = 0$

$x = \frac{-\frac{121}{4} \pm \sqrt{(\frac{121}{4})^2 - 1000}}{2}$

$x_1 = -\frac{121}{8} - 4.608j$

$x_2 = -\frac{121}{8} + 4.608j$

$V_1(t) = 8e^{-\frac{121}{8}t} (B_1 \cos 4.608t + B_2 \sin 4.608t)$

$V_1(0) = 0 \Rightarrow B_1 = 8$

$\frac{6}{25} + \frac{1}{16} = \frac{96 + 25}{400} = \frac{121}{400}$

$(\frac{121}{4})^2 - 1000$

$V_s = 0$

$\alpha < \omega$

$\alpha \approx \frac{121}{8}$

$\omega_d = 4.608$

$\alpha \approx \frac{121}{8}$

3

$\frac{d^2V}{dt^2} + \frac{121}{4} \frac{dV}{dt} + 250V = 2000$

$x^2 + \frac{121}{4}x + 250 = 0$

$x = \frac{-\frac{121}{4} \pm \sqrt{(\frac{121}{4})^2 - 1000}}{2}$

$x_1 = -\frac{121}{8} - 4.608j$

$x_2 = -\frac{121}{8} + 4.608j$

$e^{(-\frac{121}{8} - 4.608j)t} e^{(-\frac{121}{8} + 4.608j)t}$

$y(t) = C_1 e^{(-\frac{121}{8} - 4.608j)t} + C_2 e^{(-\frac{121}{8} + 4.608j)t}$

$2000, \mu = 0, n = 0 \Rightarrow m = 0$

$y_p(t) = C_0$

$y(t) = C_0 + C_1 e^{(-\frac{121}{8} - 4.608j)t} + C_2 e^{(-\frac{121}{8} + 4.608j)t}$


$= C_0 + e^{-\frac{121}{8}t} (C_1 e^{-4.608jt} + C_2 e^{4.608jt})$

$t \rightarrow \infty \quad y(t) = 8 \Rightarrow C_0 = 8V$

$y(t) = 8 + e^{-\frac{121}{8}t} (C_1 \cos 4.608t + C_2 \sin 4.608t)$

**Question 8:**

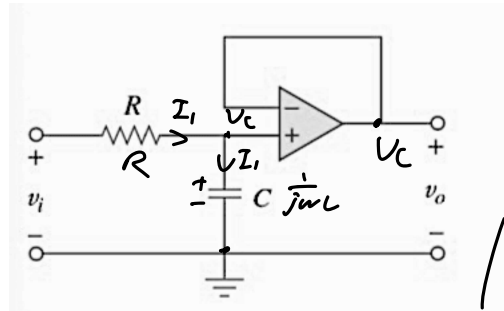- (a) Find the transfer function for the active filters in Figure 8.  
 (b) The filter in Figure 8 has a 3-dB cutoff frequency at 1 kHz. If its input is connected to a 120-mV variable frequency signal, find the output voltage at: 200 Hz, 2 kHz and 10 kHz.



$$I_1 = C \frac{dV_c}{dt}$$

$$\frac{V_i - V_c}{R} = C \frac{dV_c}{dt} \quad H(\omega) \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \cdot V_i = \frac{1}{1 + Rj\omega C} \quad \text{Figure 8}$$

$$\left( \frac{|H(1k)|^2}{|H(0)|^2} \right) = \frac{1}{2} = \frac{1}{1 + \omega^2 R^2 C^2}$$

$$1 + 1000^2 R^2 C^2 = 2 \quad 1$$

$$RC = \frac{1}{1000} \text{ s}$$

$$C \frac{dV_o}{dt} + \frac{1}{R} V_o - \frac{V_i}{R} = 0$$

$$\frac{dV_o}{dt} = -\frac{1}{RC} V_o + \frac{V_i}{RC}$$

$$V_o = 0.12 \cdot \frac{1}{1 + j\omega RC}$$

$$1 \mu\text{s} \cdot \frac{1}{1000 \text{ s}}$$

$$= 0.12 \cdot \frac{1000}{1000 + j\omega RC}$$

$$= \frac{120}{1000 + j\omega RC}$$