


**Analog Signal Processing****Thursday, March 24, 8:45-10pm****Exam II**

<b>Last Name:</b>			
<b>First Name:</b>			
<b>UIN:</b>		<b>netID:</b>	

**instructions :**

- Clearly PRINT your name in CAPITAL LETTERS.
- Clearly write your UIN and netID.
- This is a closed book and closed notes exam.
- Calculators are not allowed.
- To get credit, you must SHOW ALL your work and/or reasoning. Answers without any work or reasoning may receive no credit.
- To get full credit, simplify your answers.
- Write your final answers in the spaces provided or points may be deducted.
- All answers should INCLUDE UNITS whenever appropriate.
- The exam is printed **double-sided**.

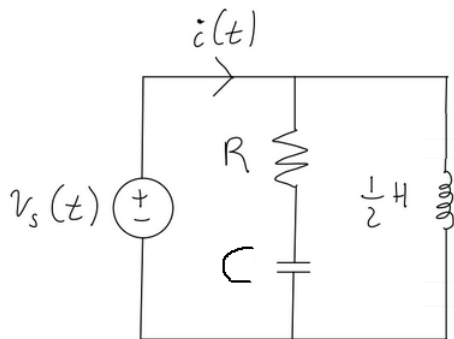1. (25 pts) Consider the LTI circuit below with voltage  $v_s(t) = \cos(2t) + \sin(2t)$  V.




- (a) [5 pts] Obtain the corresponding phasor circuit.

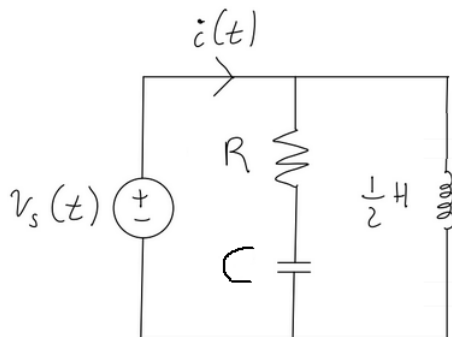- (b) [10 pts] If it is known that  $C = 1\text{F}$  and that the current  $i(t)$  is in phase with the voltage  $v_s(t)$ , determine the value of  $R$ .

$R = \underline{\hspace{2cm}}$


Recall that  $v_s(t) = \cos(2t) + \sin(2t)$  V.



- (c) [10 pts] If  $C = \frac{1}{4}$  F, and  $R = 2 \Omega$ , determine the average absorbed power in each one of the elements in the circuit.

$$P_{2\Omega} = \underline{\hspace{2cm}} \quad P_{\frac{1}{4}F} = \underline{\hspace{2cm}} \quad P_{\frac{1}{2}H} = \underline{\hspace{2cm}} \quad P_{v_s} = \underline{\hspace{2cm}}$$

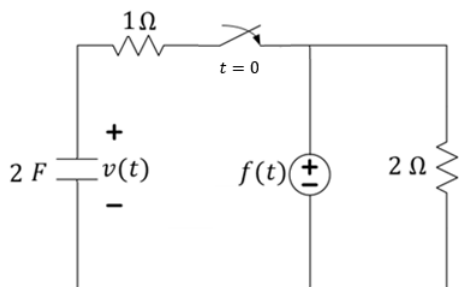2. (25 pts) Consider the circuit shown below. The switch is closed at time  $t = 0$ . The capacitor in the circuit has an initial voltage of  $v(0^-) = \frac{3}{2} V$ . The input  $f(t) = 2 \sin(\frac{1}{2}t) V$ .



- (a) [8 pts] Find the ODE of the circuit for the capacitor voltage  $v(t)$ , valid for  $t > 0$ .

ODE : \_\_\_\_\_

- (b) [12 pts] Find the particular  $v_p(t)$  and homogeneous  $v_h(t)$  solutions to the ODE.

$$v_p(t) = \underline{\hspace{10cm}}$$

$$v_h(t) = \underline{\hspace{10cm}}$$


- (c) [5 pts] Identify the transient and steady state signals that comprise the voltage of the capacitor  $v(t) = v_{tr}(t) + v_{ss}(t)$ ,  $t > 0$ .

$$v_{tr}(t) = \underline{\hspace{15cm}}$$

$$v_{ss}(t) = \underline{\hspace{15cm}}$$

3. (25 pts) The three parts of this problem are not related.

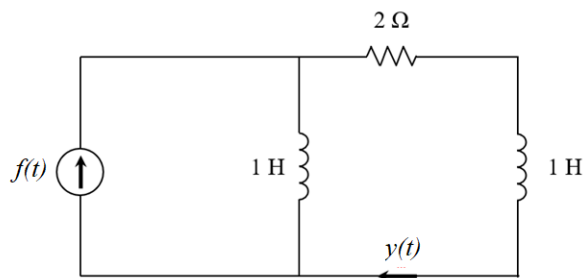(a) [6 pts] Find the frequency response,  $H(\omega)$ , of the circuit shown below.



$$H(\omega) = \underline{\hspace{10cm}}$$

(b) [11 pts] The signal  $x(t) = 2 + \cos(2t) + 2\sin(5t)$  was sent through a system having the frequency response  $H(\omega) = \frac{1}{3+3j\omega}$ . Find the output signal  $y(t)$  and express in terms of real-valued functions.

$$y(t) = \underline{\hspace{10cm}}$$


(c) [8 pts] A linear system with input  $f(t)$  and output  $y(t)$  is described by the ODE

$$\frac{d^2 y}{dt^2} + 2y = f$$

Find the frequency response of the system  $H(\omega)$  and the output signal  $y(t)$  if the input signal  $f(t) = 4 V$ .

$H(\omega) =$  \_\_\_\_\_  $y(t) =$  \_\_\_\_\_

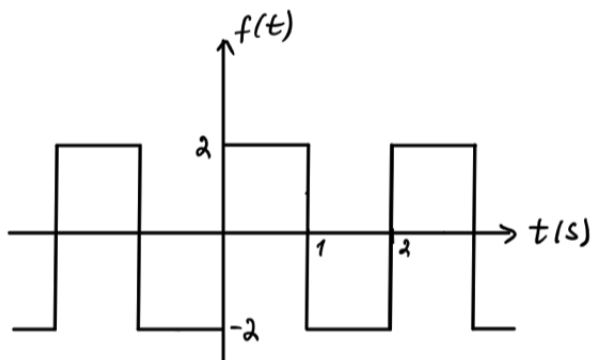4. (25 pts) Consider the periodic function  $f(t)$  given below:



Determine:

- (a) [6 pts] Period  $T$ , fundamental frequency  $\omega_0$ , and exponential Fourier series coefficient  $F_0$ .


$$T = \underline{\hspace{2cm}} \quad \omega_0 = \underline{\hspace{2cm}} \quad F_0 = \underline{\hspace{2cm}}$$

- (b) [10 pts] Exponential Fourier series of  $f(t)$ . Simplify as much as you can.

$$f(t) = \underline{\hspace{10cm}}$$



- (c) [5 pts] Let  $f(t)$  be the input to an ideal low-pass filter with magnitude response  $|H(\omega)|$  and phase response  $\angle H(\omega)$  given below. Determine the steady-state output  $y(t)$ .

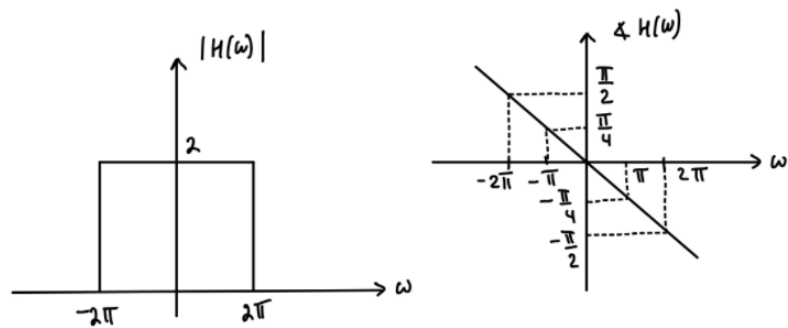

$$y(t) = \underline{\hspace{10cm}}$$

- (d) [4 pts] Express  $y(t)$  in terms of real-valued functions.

$$y(t) = \underline{\hspace{10cm}}$$

You may use this sheet for additional calculations but **do not** separate this sheet from the rest of the exam.

You may use this sheet for additional calculations but **do not** separate this sheet from the rest of the exam.