

ECE 210/211: Exam 2
Wednesday, October 19, 2022

Name: (in BLOCK CAPITALS) _____


UIN: _____

NetID: _____

Instructions

- Clearly PRINT your name in CAPITAL LETTERS.
- Clearly write your UIN and netID.
- This is a closed book and closed notes exam.
- Calculators and other electronic devices are not allowed.
- To get credit, you must SHOW ALL your work and provide explanations when needed.
- To get full credit, simplify your answers.
- All answers must INCLUDE UNITS whenever appropriate.
- Angles must be expressed in the range $(-\pi, \pi]$ rad.
- Write your final answers in the spaces provided or points may be deducted.
- The exam is printed double-sided.
- There is an empty page at the end of the exam in case you need additional space.

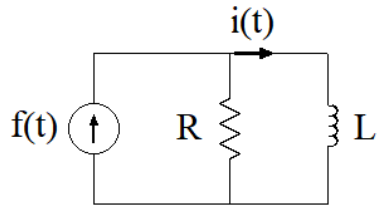1. [25 points] Consider the following circuit for $t > 0$.



- (a) [5 pts] Obtain the ODE that governs this system for $t > 0$ in terms of R , L , $i(t)$ and $f(t)$ only (no other variables).

ODE = _____

For the rest of the problem, let $R = 8 \, \Omega$, $f(t) = \frac{1}{2} \cos(\omega t) + 2 \sin(\omega t)$ A and $i(0^-) = -1$ A. It is known that $i(t) = B e^{-4t} - \frac{2}{5} \cos(2t) + \frac{9}{5} \sin(2t)$ A for $t > 0$.

- (b) [5 pts] Determine the values of L and ω .

$L =$ _____ $\omega =$ _____

Recall that $R = 8 \, \Omega$, $f(t) = \frac{1}{2} \cos(\omega t) + 2 \sin(\omega t)$ A and $i(0^-) = -1$ A. It is known that for $t > 0$, $i(t) = Be^{-4t} - \frac{2}{5} \cos(2t) + \frac{9}{5} \sin(2t)$ A.

- (c) [5 pts] If $i(t)$ is the zero-state response, what is the value of B ?

$$B = \underline{\hspace{2cm}}$$

- (d) [5 pts] If $B = -\frac{3}{5}$ when $i(t)$ is the full solution of the ODE, determine $i_{tr}(t)$, the transient component of $i(t)$ and also determine $i_{ss}(t)$, the steady-state component of $i(t)$.

$$i_{tr}(t) = \underline{\hspace{4cm}} \quad i_{ss}(t) = \underline{\hspace{4cm}}$$

- (e) [5 pts] Determine the steady-state phasor I .

$$I = \underline{\hspace{2cm}}$$

2. [12 points] Let a dissipative LTI system have frequency response $H(\omega) = \frac{Y}{F} = \frac{j\omega}{1-\omega^2+j\omega}$ where F and Y are the phasors of the input $f(t)$ and output $y(t)$, respectively.

(a) [3 pts] Determine $|H(\omega)|$.

$$|H(\omega)| = \frac{|\omega|}{\sqrt{\omega^4 - \omega^2 + 1}} \quad \omega^2 \neq 1 - 2\omega^2 + \omega^4$$

$$\frac{2j}{-3+2j}$$

$$|H(\omega)| = \underline{\hspace{2cm}}$$

- (b) [9 pts] Let $f(t) = 2 + \cos(t + \frac{\pi}{4}) + 2\sin(2t)$. Determine the steady-state output, $y_{ss}(t)$.

$$\text{for } 2 \quad \omega=0 \quad \angle = 0$$

$$\text{for } \cos(t + \frac{\pi}{4}) \quad \angle(1) = 45^\circ$$

$$\angle(1) = 45^\circ$$

$$\text{for } 2\sin(2t) \quad \angle(2) = 2 \quad \angle(2) = \frac{4j}{-3+2j}$$

$$\angle(2) = \frac{4}{\sqrt{13}} \cdot \angle(90 + \arctan \frac{2}{3})$$


=

$$y_{ss}(t) = \cos(t + 45^\circ)$$

$$+ \frac{4}{\sqrt{13}} \cos(2t + 90 + \arctan \frac{2}{3})$$

$$y_{ss}(t) = \underline{\hspace{2cm}}$$

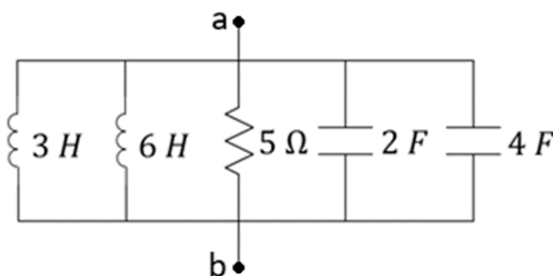3. [13 points] Consider the circuit shown below.



- (a) [3 pts] What is the impedance of just the two inductors (3 H and 6 H) in parallel as a function of ω ?

$Z_{L,eq} =$ _____


- (b) [3 pts] What is the impedance of just the two capacitors (2 F and 4 F) in parallel as a function of ω ?

$Z_{C,eq} =$ _____

- (c) [7 pts] At what frequency $\omega > 0$ does the circuit shown above have a real-valued equivalent impedance between nodes **a** and **b**?

$\omega =$ _____

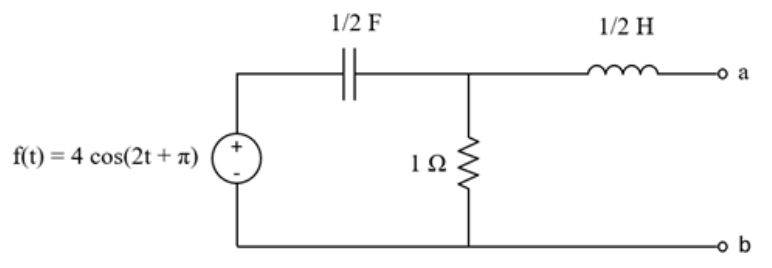4. [18 points] Consider the circuit below.




- (a) [5 pts] Determine the voltage phasor across the capacitor, and identify its magnitude and phase.

$|V_C| = \underline{\hspace{2cm}} \quad \angle V_C = \underline{\hspace{2cm}}$

- (b) [3 pts] Determine the average absorbed power in the capacitor, P_C .

$P_C = \underline{\hspace{2cm}}$

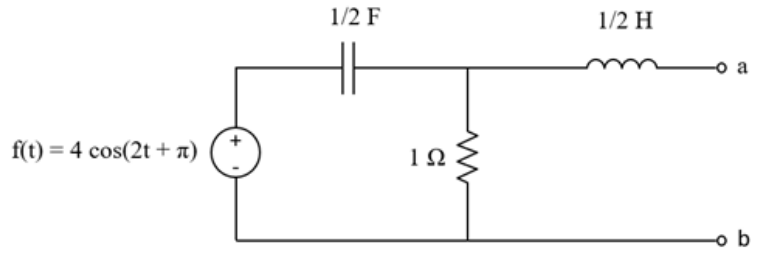


- (c) [5 pts] Determine the Thevenin's equivalent voltage phasor of this circuit as seen from terminals a and b , and identify its magnitude and phase.

$|V_T| = \underline{\hspace{2cm}} \quad \angle V_T = \underline{\hspace{2cm}}$

- (d) [5 pts] Determine the Thevenin's equivalent impedance, express it in rectangular form, and simplify it as much as you can.

$Z_T = \underline{\hspace{2cm}}$

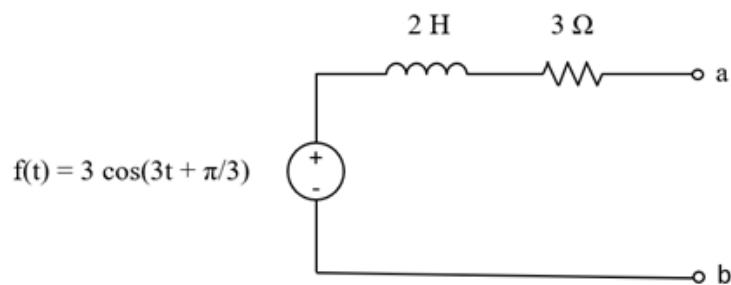5. [7 points] Consider the circuit below.



- (a) [5 pts] Determine the maximum average absorbed power that the circuit may deliver to a load.

$P_{max} =$ _____

- (b) [2 pts] Determine the maximum average absorbed power that the circuit may deliver to a load if the inductor is replaced by a capacitor having capacitance $C = 5$ F.

$P_{max} =$ _____

6. [6 points] Given the periodic function $f(t) = 4\sin^2(3t - \frac{\pi}{3})$, write out all of the non-zero Fourier series coefficients F_n that describe its Fourier expansion in exponential form.

Hint: $\sin(\theta) = \frac{e^{j\theta} - e^{-j\theta}}{2j}$.

$\omega = 6 \quad T = \frac{2\pi}{6} = \frac{\pi}{3}$

$$F_n = \frac{1}{T} \int_0^T f(t) e^{-jn\omega t} dt$$

$$= \frac{3}{2\pi} \int_0^{\frac{\pi}{3}} 4\sin^2(3t - \frac{\pi}{3}) e^{-3jn\omega t} dt$$

$$2 - 2\cos(6t - \frac{2\pi}{3}) = \frac{3}{2\pi} \left(\int_0^{\frac{\pi}{3}} 2 e^{-3jn\omega t} dt + \int_0^{\frac{2\pi}{3}} -2 \cos(6t - \frac{2\pi}{3}) e^{-3jn\omega t} dt \right)$$

$$\frac{1 - \cos(6t - \frac{2\pi}{3})}{2} \cdot 4 = \frac{3}{2\pi} \left(-\frac{2}{3jn} e^{-3jn\omega t} \Big|_0^{\frac{\pi}{3}} + \int_0^{\frac{2\pi}{3}} \frac{j}{2} \cdot \frac{e^{j(6t - \frac{2\pi}{3})} - e^{j(-6t + \frac{2\pi}{3})}}{2j} e^{-3jn\omega t} dt \right)$$

$$= \frac{3}{2\pi} \left(-\frac{2}{3jn} e^{-\pi jn} + \frac{2}{3jn} + j \left(\frac{e^{\frac{\pi}{6}j}}{6j} (e^{4\pi j} - 1) + \frac{e^{\frac{\pi}{6}j}}{6j} (e^{-4\pi j} - 1) \right) \right)$$

$$= \frac{3}{2\pi} \left(j \left(e^{-\frac{\pi}{6}j} (e^{(6j-3jn)t}) - e^{\frac{\pi}{6}j} e^{-(6j+3jn)t} \right) \right) dt$$


$$= \frac{3}{2\pi} \left(j \left(\frac{e^{-\frac{\pi}{6}j}}{6j-3jn} (e^{2\pi j - 1\pi jn} - 1) + \frac{e^{\frac{\pi}{6}j}}{6j+3jn} (e^{-2\pi j - 1\pi jn} - 1) \right) \right)$$

$$= \frac{3}{2\pi} \left(\frac{e^{-\frac{\pi}{6}j}}{6-3n} \right) \quad n=1$$

$$\begin{cases} \frac{3}{2\pi} \left(\frac{e^{-\frac{\pi}{6}j}}{6-3n} \right) & n \text{ is odd} \\ \frac{1}{\pi} \left(\frac{e^{-\frac{\pi}{6}j}}{n-2} - \frac{e^{\frac{\pi}{6}j}}{2+n} \right) & n \text{ is odd} \end{cases}$$

$$F_n = \frac{2}{\pi jn} + \frac{1}{\pi} \left(\frac{e^{\frac{\pi}{6}j}}{n-2} - \frac{e^{\frac{\pi}{6}j}}{2+n} \right) \quad n \text{ is odd}$$

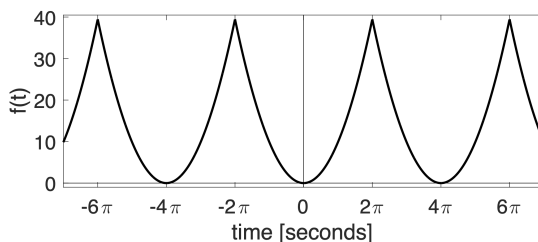7. [19 points] Consider the periodic signal $f(t)$ which equals t^2 over the range $-2\pi < t < 2\pi$ as shown in the figure below. This signal can be expressed as a Fourier series expansion having exponential coefficients F_0 and $F_{n \neq 0} = \frac{8}{n^2}(-1)^n$.



- (a) [2 pts] What is the fundamental frequency, ω_0 , of signal $f(t)$?

$$T = 4\pi \quad \omega = \frac{2\pi}{T} = \frac{1}{2}$$

$$\omega_0 = \frac{1}{2}$$

- (b) [4 pts] What is F_0 ?

$$\begin{aligned} F_0 &= \frac{1}{T} \int_{-2\pi}^{2\pi} t^2 dt \\ &= \frac{1}{4\pi} \left[\frac{28\pi^3}{3} \right] \cdot 2 = \frac{4\pi^2}{3} \end{aligned}$$

$$F_0 = \frac{4\pi^2}{3}$$

- (c) [5 pts] Write out the Fourier series expansion of $f(t)$ as an approximation comprised of the superposition of five terms corresponding to $n = -2, -1, 0, 1, 2$.

$$f(t) = \frac{4\pi^2}{3} - 8e^{j2t} - 8e^{-j2t} + 2e^{jt} + 2e^{-jt}$$

$$f(t) \approx \underline{\hspace{10cm}}$$

- (d) [2 pts] Periodic signals can also be expressed in terms of trigonometric functions via the following general form:

$$f(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} [a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)]$$

For the $f(t)$ shown above, which of the following statements is true? Briefly explain your answer.

- i. $a_n = 0$ and $b_n \neq 0$ for all n
- ii. $a_n \neq 0$ and $b_n = 0$ for all n ✓
- iii. $a_n \neq 0$ and $b_n \neq 0$ for all n

Explain: ii even function

- (e) [6 pts] Now consider this signal as input to an LTI system characterized by frequency response $H(\omega) = \frac{j\omega}{2+j\omega}$, such that the output $y(t)$ can also be expressed as a Fourier series having coefficients Y_n . What are the magnitude and phase of the Y_2 coefficient?

for $n=2$ $\omega_2 = 2$ $H(1) = \frac{j}{2+j}$

$$Y_2 = \frac{4j}{2+j}$$

$$\frac{4 \times 2}{2\sqrt{2}}$$

$$|Y_2| = \sqrt{2}$$

$$90^\circ - 45^\circ$$

$$\phi = 45^\circ \quad \frac{2}{\sqrt{2}}$$

$$90^\circ - \arctan \frac{1}{2}$$

$|Y_2| =$ _____ $\angle Y_2 =$ _____

You may use this sheet for additional calculations but do not separate this sheet from the rest of the exam.

You may use this sheet for additional calculations but do not separate this sheet from the rest of the exam.